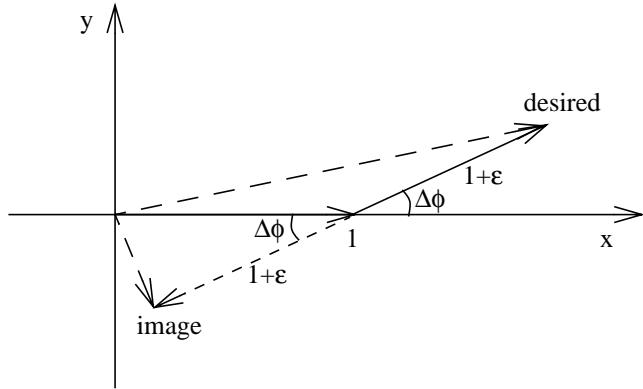


Solutions exercise 1 (Architectures)

1. Problem 18.3 (also problem 2a exam 01-03-06):



$$\begin{aligned}
 IRR &= \frac{(x\text{-composant desired})^2 + (y\text{-composant desired})^2}{(x\text{-composant image})^2 + (y\text{-composant image})^2} \\
 &= \frac{[1 + (1 + \varepsilon)\cos\Delta\phi]^2 + [(1 + \varepsilon)\sin\Delta\phi]^2}{[1 - (1 + \varepsilon)\cos\Delta\phi]^2 + [(1 + \varepsilon)\sin\Delta\phi]^2} = \frac{1 + 2(1 + \varepsilon)\cos\Delta\phi + (1 + \varepsilon)^2}{1 - 2(1 + \varepsilon)\cos\Delta\phi + (1 + \varepsilon)^2}
 \end{aligned}$$

The numerator is approximately equal to 4 for small ε and $\Delta\phi$.

The denominator $N(\Delta\phi, \varepsilon)$ is expanded in a Taylor series around $(\Delta\phi, \varepsilon) = (0, 0)$:

$$\frac{\partial N}{\partial \Delta\phi} = 2(1 + \varepsilon)\sin\Delta\phi = 0, \quad \Delta\phi = \varepsilon = 0$$

$$\frac{\partial N}{\partial \varepsilon} = -2\cos\Delta\phi + 2 + 2\varepsilon = 0, \quad \Delta\phi = \varepsilon = 0$$

$$\frac{\partial^2 N}{\partial \Delta\phi \partial \varepsilon} = 2\sin\Delta\phi = 0, \quad \Delta\phi = \varepsilon = 0 \quad \Rightarrow \quad N \approx (\Delta\phi)^2 + \varepsilon^2$$

for small ε and $\Delta\phi$

$$\frac{\partial^2 N}{\partial (\Delta\phi)^2} = 2(1 + \varepsilon)\cos\Delta\phi = 2, \quad \Delta\phi = \varepsilon = 0$$

$$\frac{\partial^2 N}{\partial \varepsilon^2} = 2$$

That is

$$IRR \approx \frac{4}{(\Delta\phi)^2 + \varepsilon^2} \quad \text{for small } \varepsilon \text{ and } \Delta\phi$$

Problem 2 (also problem 2b exam 01-03-06)

Bluetooth:

$$IRR = 20dB = 100 = \frac{4}{(\Delta\phi)^2 + \epsilon^2} \Rightarrow (\Delta\phi)^2 + \epsilon^2 = \frac{1}{25} \Rightarrow \Delta\phi \text{ or } \epsilon = \frac{1}{5}$$

$$\Delta\phi = \frac{1}{5}\text{rad} = \frac{1}{5} \cdot \frac{180}{\pi} = 11^\circ \quad \text{or} \quad \epsilon = \frac{1}{5} = 20\%$$

This matching accuracy can easily be achieved in an integrated circuit.

Mobile phone:

$$IRR = 80dB = 10^8 = \frac{4}{(\Delta\phi)^2 + \epsilon^2} \Rightarrow (\Delta\phi)^2 + \epsilon^2 = \frac{4}{10^8} \Rightarrow \Delta\phi \text{ or } \epsilon = 2 \cdot 10^{-4}$$

$$\Delta\phi = 0.011^\circ \quad \text{or} \quad \epsilon = \frac{1}{5} = 0.020\%$$

This is very difficult (or impossible) to achieve

3. Problem 18.6 with extension

$$\text{Cubic nonlinearity: } v_o = a_0 + a_1 v_i + a_2 v_i^2 + a_3 v_i^3$$

$$\text{IIP}_2: \quad |a_1 v_i| = |a_2 v_i^2| \Rightarrow |v_i| = \left| \frac{a_1}{a_2} \right| \Rightarrow IIP_2 = \frac{1}{R_{in}} \cdot \left(\frac{a_1}{a_2} \right)^2$$

$$\text{IIP}_3: \quad |a_1 v_i| = |a_3 v_i^3| \Rightarrow v_i^2 = \left| \frac{a_1}{a_3} \right| \Rightarrow IIP_3 = \frac{1}{R_{in}} \cdot \left| \frac{a_1}{a_3} \right|$$

$$\Rightarrow \frac{IIP_2}{IIP_3} = \left| \frac{a_1^2/a_2^2}{a_1/a_3} \right| = \left| \frac{a_1 a_3}{a_2^2} \right|$$


Extension. Assume $a_1 > 0, a_2 = 0, a_3 < 0$

ICP (1dB):

$$a_1 v_i - |a_3| v_i^3 = a_1 v_i \cdot 10^{-\frac{1}{20}} \Rightarrow a_1 v_i \left(1 - 10^{-\frac{1}{20}} \right) = |a_3| v_i^3 \Rightarrow ICP = \frac{1}{R_{in}} \cdot \left| \frac{a_1}{a_3} \right| \cdot \left(1 - 10^{-\frac{1}{20}} \right)$$

$$\Rightarrow \frac{IIP_3}{ICP} = \frac{1}{\left(1 - 10^{-\frac{1}{20}} \right)} = 9.2 = 9.6\text{dB}$$

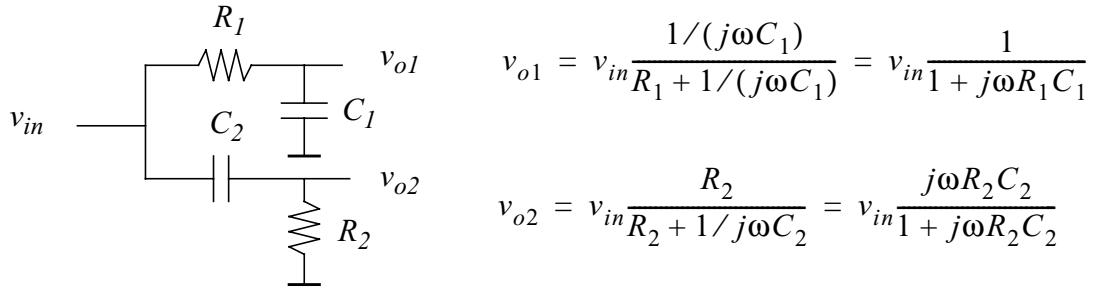4. Phase difference versus frequency of RC-CR link



$$\frac{v_{o1}}{v_{o2}} = \frac{1}{j\omega R_2 C_2} \cdot \frac{1 + j\omega R_2 C_2}{1 + j\omega R_1 C_1} = \{R_1 C_1 = R_2 C_2 = RC\} = \frac{1}{j\omega RC}$$

If the time constants are selected equal, the phase difference is 90 degrees at all frequencies!

5. Design of RC-CR (problem 1 exam 010306 with extension)

See figure above. $R_1 = R_2 = 500\Omega$. Equal time constant give equal capacitors as well. To get equal amplitudes $\omega_0 RC$ must be equal to unity:

$$\omega_0 RC = 1 \Rightarrow C = \frac{1}{\omega_0 R} = \frac{1}{2\pi \cdot 10^9 \cdot 500} = 0.32\text{pF}$$

$$\left| \frac{v_{o2}}{v_{o1}} \right| = \omega RC = \frac{\omega}{\omega_0} = \frac{f}{f_0} \quad 0.95 < \frac{f}{f_0} < 1.05 \Rightarrow 950\text{MHz} < f < 1.05\text{GHz}$$

$$\text{unloaded at } \omega_0: Z_{in} = \frac{1}{2} \left(R + \frac{1}{j\omega_0 C} \right) = \frac{1}{2} \left(R + \frac{RC}{jC} \right) = \frac{1}{2} (R - jR) = 250(1 - j) \Omega$$

What happens when the outputs are loaded by $5\text{k}\Omega$ each?


$$v_{o1} = v_{in} \frac{\frac{10R \cdot 1/sC}{10R + 1/sC}}{R + \frac{10R \cdot 1/sC}{10R + 1/sC}} = v_{in} \frac{\frac{10R \cdot \frac{1}{sC}}{10R + \frac{1}{sC}}}{\left(10R + \frac{1}{sC}\right)R + 10R \cdot \frac{1}{sC}} = v_{in} \frac{10R}{(1 + 10sRC)R + 10R}$$

$$= v_{in} \frac{10}{1 + 10sRC + 10} = v_{in} \frac{1}{\frac{11}{10} + sRC}$$

$$v_{o2} = v_{in} \frac{\frac{10R}{11} \cdot \frac{10}{11}sRC}{\frac{10}{11}R + \frac{1}{sC}} = v_{in} \frac{\frac{10}{11}sRC}{\frac{10}{11}sRC + 1} = v_{in} \frac{sRC}{\frac{10}{11} + sRC} \quad \frac{v_{o2}}{v_{o1}} = sRC = j\omega RC$$

The outputs are still in quadrature and have equal amplitudes. The only difference is that the amplitude is reduced slightly (5%) by the loading.

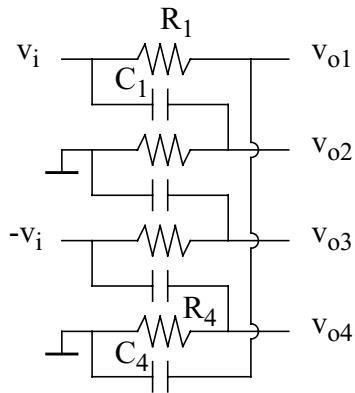6,7 Absolute and relative mismatch in a single stage polyphase filter



$$\begin{aligned}
 v_{o1} &= v_i \cdot \frac{1/sC_4}{1/sC_4 + R_1} = v_i \cdot \frac{1}{1 + sR_1C_4} \\
 v_{o2} &= v_i \cdot \frac{R_2}{1/sC_1 + R_2} = v_i \cdot \frac{sR_2C_1}{1 + sR_2C_1} \\
 v_{o3} &= -v_i \cdot \frac{1/sC_2}{1/sC_2 + R_3} = -v_i \cdot \frac{1}{1 + sR_3C_2} \\
 v_{o4} &= -v_i \cdot \frac{R_4}{1/sC_3 + R_4} = -v_i \cdot \frac{sR_4C_3}{1 + sR_4C_3}
 \end{aligned}$$

6. Absolute error:

No phase error will occur if all resistors and capacitors are equal (perfectly matched).

20% absolute error =>

$$\text{amplitude error} = \left| \frac{v_{o2}}{v_{o1}} \right| - 1 = \omega_0 RC - 1 = \left\{ RC = \frac{1}{\omega_0} \pm 20\% \right\} = \pm 20\%$$

7. Mismatch:

If **one** capacitor is 0.2% off, just **one** output signal will be affected.

$$\text{phase error} = \angle(1 + j\omega_0 RC_{nom}) - \angle(1 + j\omega_0 RC) = \left\{ \omega_0 = \frac{1}{RC_{nom}} \right\}$$

$$= \angle(1 + j) - \angle(1 + (j \pm 0.2\%)) = 0.06^\circ$$