

Solutions exercise 4 (Noise)

1. Problem 10.6

a.

$$R_{opt} = \frac{v_n}{i_n}$$

$$\text{Amplifier A: } R_{opt} = \frac{10\text{nV}}{50\text{fA}} = 200\text{k}\Omega \quad \text{Amplifier B: } R_{opt} = \frac{10\text{nV}}{100\text{fA}} = 100\text{k}\Omega$$

b. Use amplifier A and transform to 200kΩ. (Also without transformer, A gives less noise)

c.

$$\left. \begin{aligned} F_{min} &= 1 + 2 \cdot \frac{R_n}{R_{opt}} \\ R_n &= \frac{\overline{v_n^2}}{4kT\Delta f} = \frac{(10 \cdot 10^{-9})^2}{4 \cdot 4.00 \cdot 10^{-21}} = 6.25\text{k}\Omega \end{aligned} \right\} \Rightarrow F_{min} = 1 + 2 \cdot \frac{6.25}{200} = 1.065 = 0.3\text{dB}$$

2. Problem 10.9

Given: $A_v = 1000$ $BW = 1\text{kHz}$, single pole


a. $\overline{v_{n,out}^2} = \overline{v_{ni}^2} \cdot A_v^2 \cdot BW \cdot \frac{\pi}{2} = 10^{-15} \cdot 10^6 \cdot 10^3 \cdot \frac{\pi}{2} = 1.57 \cdot 10^{-6} \text{ V}^2$

b. $\overline{v_{ni}^2} = 10^{-15} \cdot \left(1 + \frac{10\text{Hz}}{f}\right) \cdot \Delta f$ The same noise as in (a) plus additional 1/f-noise

$$\overline{v_{n,out,1/f}^2} \approx \int_{f_0}^{1000} 10^{-14} \cdot \frac{1}{f} df \cdot A_v^2 = 10^{-14} \cdot 10^6 \cdot \ln\left(\frac{1000}{f_0}\right)$$

$$f_0 = 1\text{mHz} \Rightarrow \overline{v_{n,out,1/f}^2} \approx 10^{-8} \cdot \ln(10^6) = 1.4 \cdot 10^{-7} \text{ V}^2 \Rightarrow \overline{v_{n,out}^2} = 1.57 \cdot 10^{-6} + 1.4 \cdot 10^{-7} = 1.7 \cdot 10^{-6} \text{ V}^2$$

3. Problem 10.11

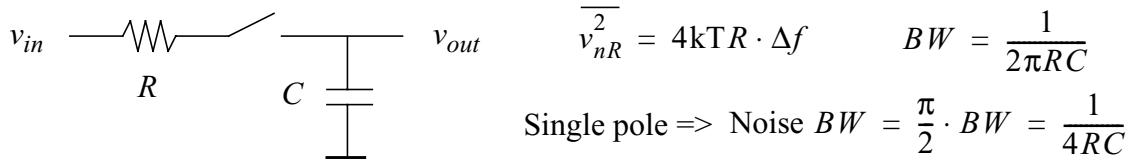


$$\text{Total noise} = \overline{v_{nR}^2} \cdot \text{Noise } BW = 4kTR \cdot \frac{1}{4RC} = \frac{kT}{C}$$

The total noise only depends on C (independent of R). This is an important result for switched capacitor circuits.

4. Problem 10.12


First study the single-ended case:

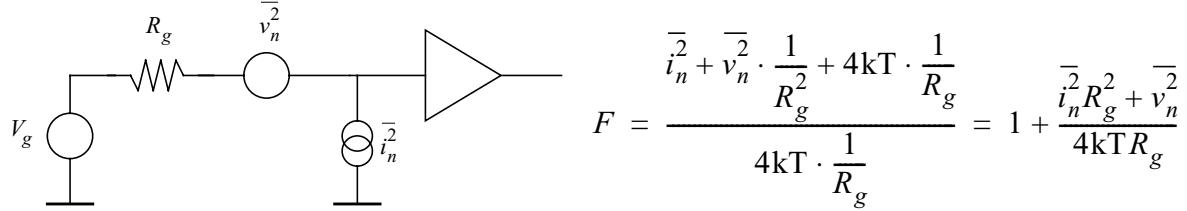

$$\frac{\partial F}{\partial R_g} = \frac{\bar{i}_n^2}{4kT} - \frac{\bar{v}_n^2}{4kT} \cdot \frac{1}{R_g^2} = 0 \Rightarrow R_{g, opt} = \sqrt{\bar{v}_n^2 / \bar{i}_n^2}$$

$$F_{min} = 1 + \frac{\bar{i}_n^2 R_{g, opt}^2 + \bar{v}_n^2}{4kTR_{g, opt}} = 1 + \frac{\bar{i}_n^2 (\bar{v}_n^2 / \bar{i}_n^2) + \bar{v}_n^2}{4kT \sqrt{\bar{v}_n^2 / \bar{i}_n^2}} = 1 + \frac{2 \cdot \bar{v}_n^2}{4kT} \cdot \sqrt{\bar{i}_n^2 / \bar{v}_n^2} = 1 + \frac{2 \sqrt{\bar{v}_n^2 \cdot \bar{i}_n^2}}{4kT}$$

Now move on to the differential one:

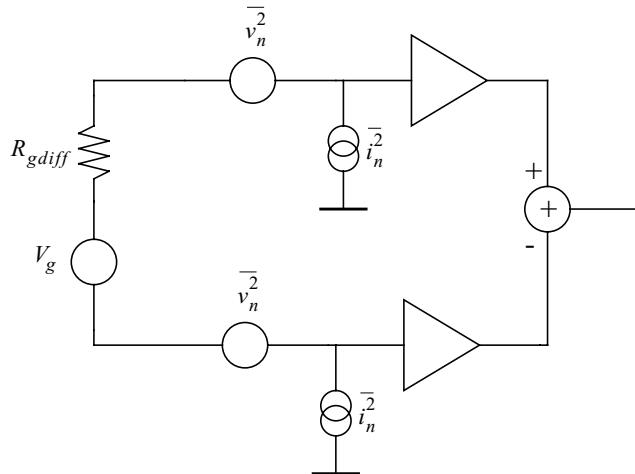

$$F = \frac{2 \cdot \bar{i}_n^2 + 2 \cdot 4 \cdot \bar{v}_n^2 / R_{gdiff}^2 + 4 \cdot 4kT / R_{gdiff}}{4 \cdot 4kT / R_{gdiff}} = \frac{2 \cdot \bar{i}_n^2 \cdot R_{gdiff}^2 + 8 \cdot \bar{v}_n^2 + 16kT \cdot R_{gdiff}}{16kT \cdot R_{gdiff}}$$

$$= \frac{\bar{i}_n^2 \cdot R_{gdiff}^2 + 4 \cdot \bar{v}_n^2 + 8kT \cdot R_{gdiff}}{8kT \cdot R_{gdiff}} = 1 + \frac{\bar{i}_n^2 \cdot R_{gdiff}^2 + 4 \cdot \bar{v}_n^2}{8kT \cdot R_{gdiff}}$$

$$\frac{\partial F}{\partial R_{gdiff}} = \frac{\bar{i}_n^2}{8kT} - \frac{\bar{v}_n^2}{2kT \cdot R_{gdiff}^2} = 0 \Rightarrow R_{gdiff, opt} = 2 \cdot \sqrt{\bar{v}_n^2 / \bar{i}_n^2} = 2 \cdot R_{g, se, opt}$$

$$F_{min} = 1 + \frac{\bar{i}_n^2 \cdot R_{gdiff, opt}^2 + 4 \cdot \bar{v}_n^2}{8kT \cdot R_{gdiff, opt}} = \dots = 1 + \frac{2 \sqrt{\bar{v}_n^2 \cdot \bar{i}_n^2}}{4kT} = F_{min, se}$$

Result: The optimum differential source resistance is twice the optimum single ended resistance, and the minimum **noise figure is the same in both cases**.