

Interferer Robust Wide-band Receiver Techniques

Bram Nauta

University of Twente

The Netherlands

<http://icd.ewi.utwente.nl>


b.nauta@utwente.nl

UNIVERSITY OF TWENTE.

Outline

- Introduction
- Interferer robust SDR RX – analog part
- Interferer robust SDR RX – digital part
- Mixer-first RX
- N-path RF filter
- Interferer scrambler for Software Radio

 Preferred: one wide band frontend IC: Software Defined



Keep minimal

RF system trend (I)

- Challenges **wide band** circuits:

Minimal pre-filtering:



high linearity

No high Q tanks:



low noise

- Bandwidth will be ok for low GHz
- Towards Software Defined Radio


Outline

- Introduction
- **Interferer robust SDR RX – analog part**
- Interferer robust SDR RX – digital part
- Mixer-first RX
- N-path RF filter
- Interferer scrambler for Software Radio

A Software-Defined Radio
Receiver Architecture
Robust to Out-of-Band Interference


[Ru, ISSCC 2009]

Conventional Multi-Band Receiver

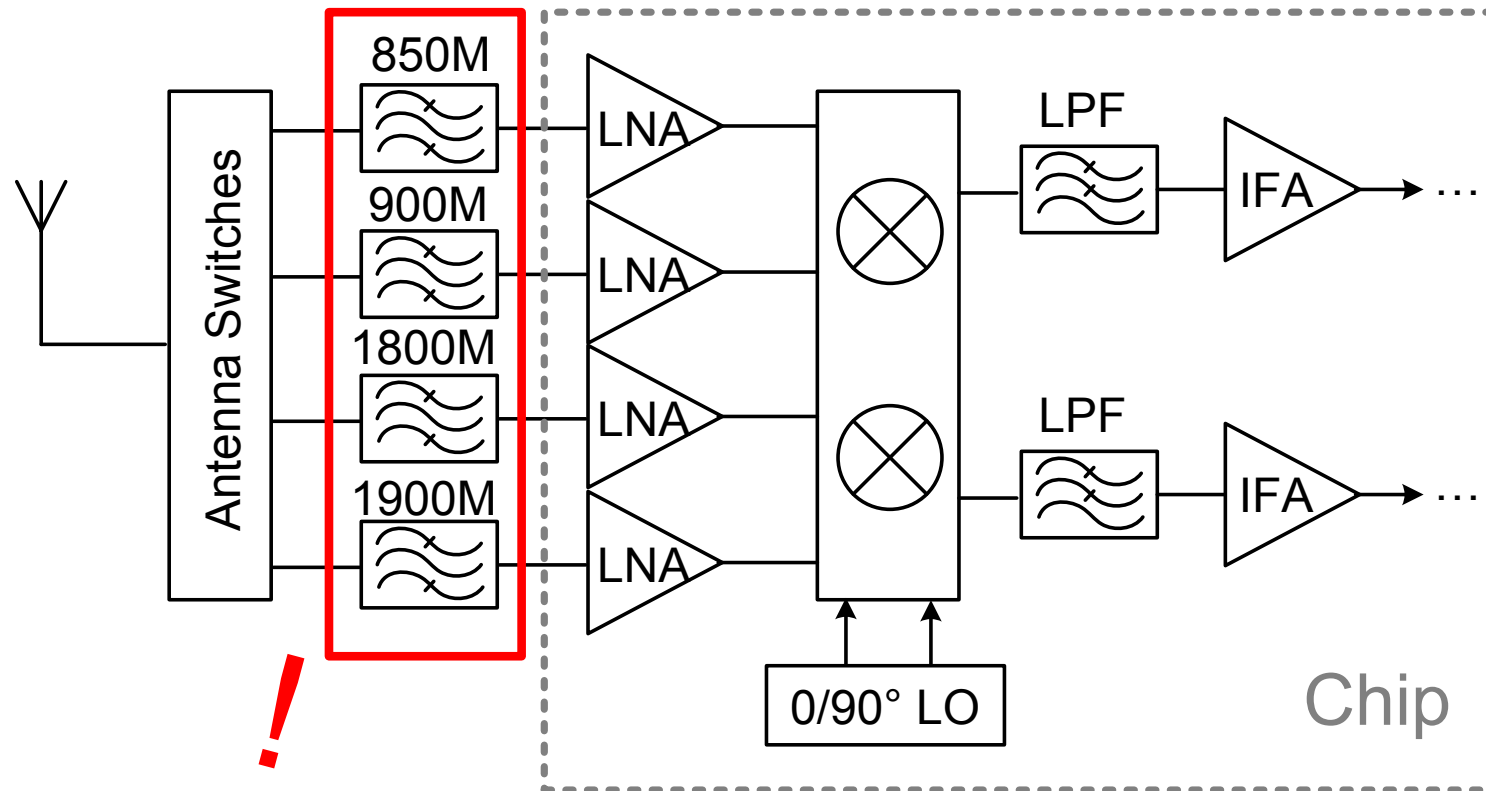


- RF filters for out-of-band interference, but bulky, costly, lossy, inflexible...
- **Our goal: Software Defined Radio with relaxed RF filtering**

Wideband Interfering: Nonlinearity

 


- Wideband LNA: also amplifies interference → nonlinearity

Wideband Interfering: Harmonic Mixing

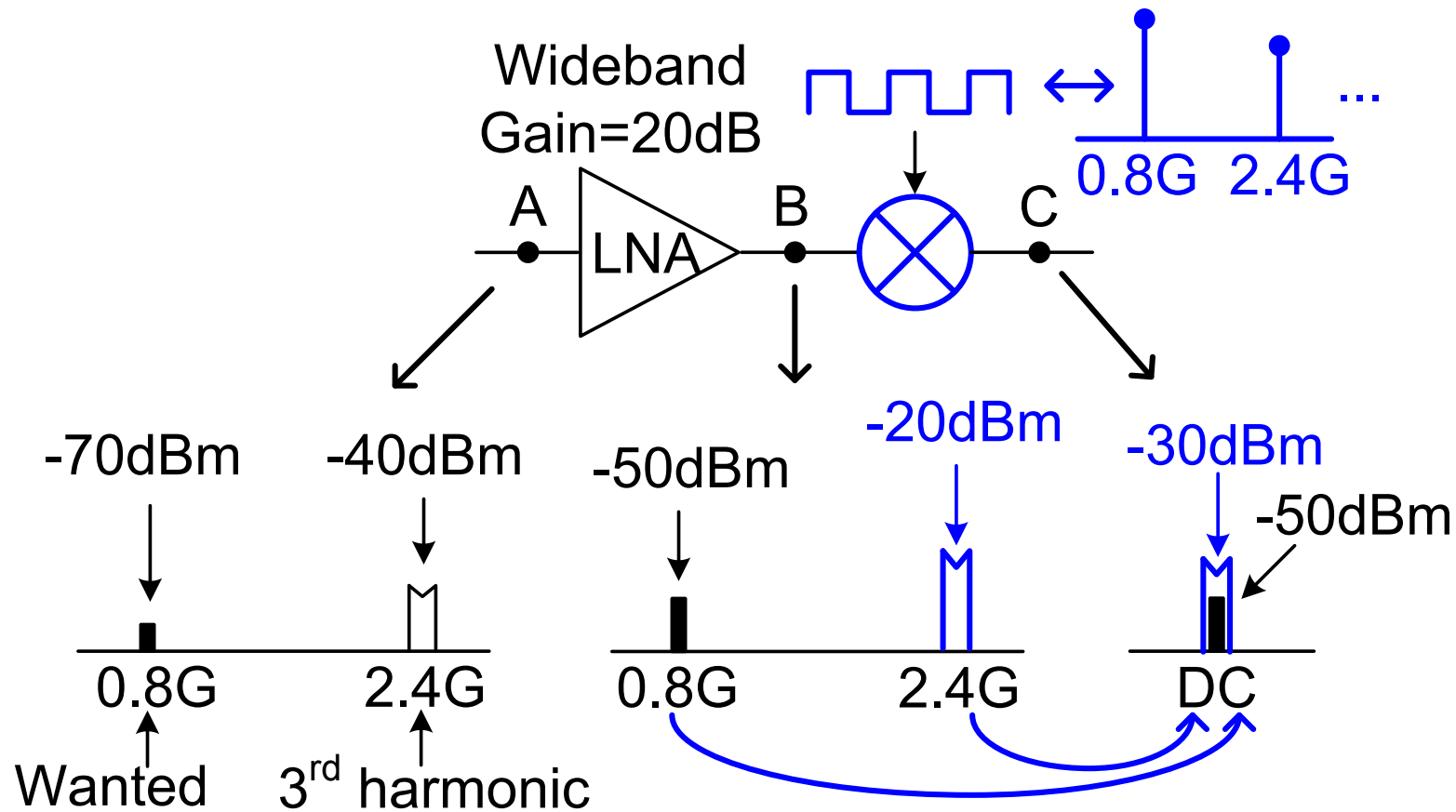


- Switching mixer: square-wave LO → harmonic mixing

 Concept: Use LP Filtering for Selectivity



- Voltage gain only at BB after low-pass filter (LPF) to filter blockers
 - Keep low impedance over a wide band at node B


Realization: Wideband LNTA + Mixer + TIA

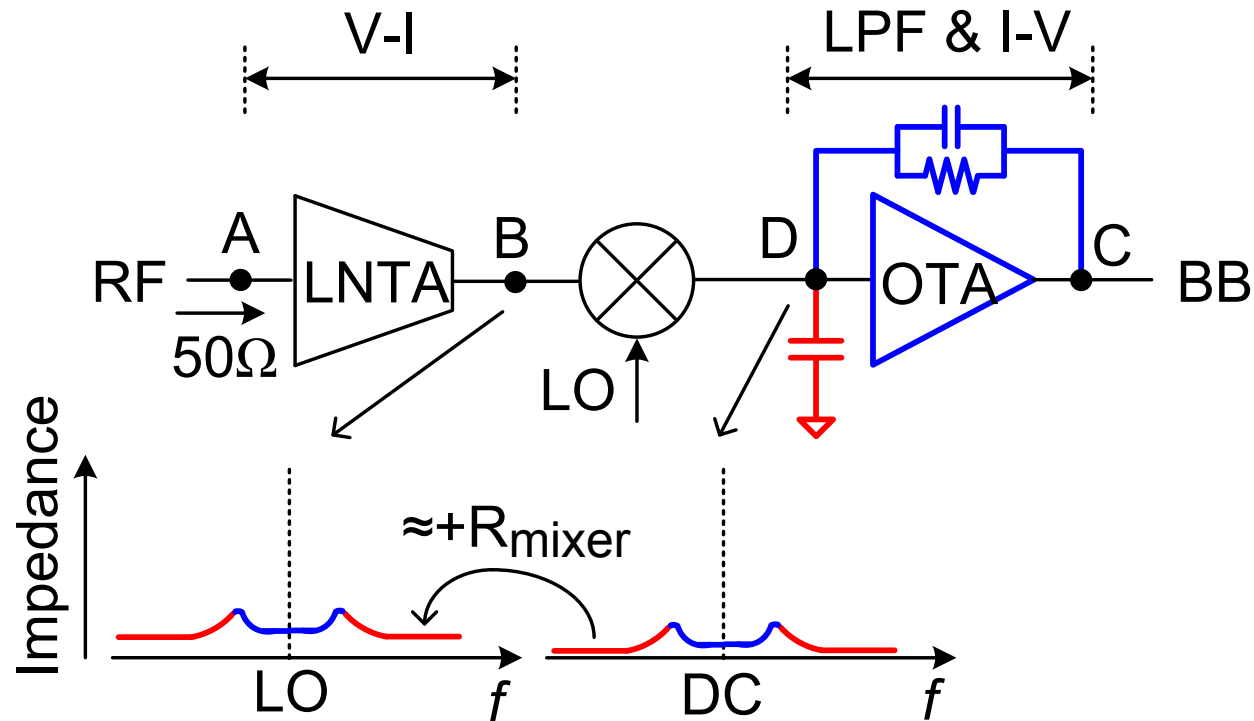

- LNTA: high G_m & high R_{out} \rightarrow low noise
small voltage swing at node B \rightarrow good linearity
- Similar to [1], but now wideband and with blocker filtering

[1] Redman-White & Leenaerts, ESSCIRC07

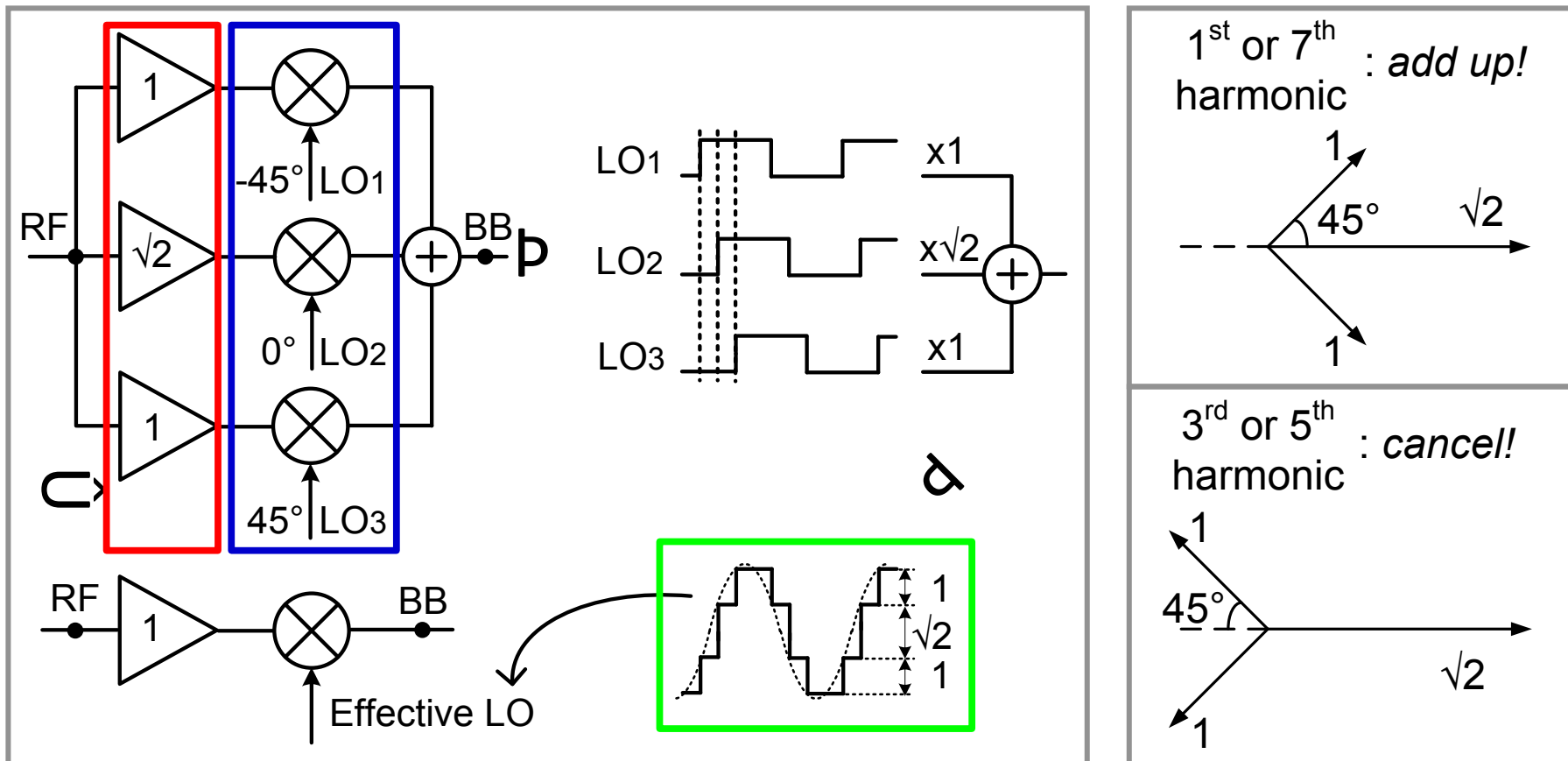Harmonic Rejection (HR) Mixer: Remove 3LO and 5LO




- Amplitude weighting + phase shifting → emulate sine-LO

[2] Weldon et. al., ISSCC01


Problem: Amplitude and Phase Errors

3rd or 5th harmonic vector diagram

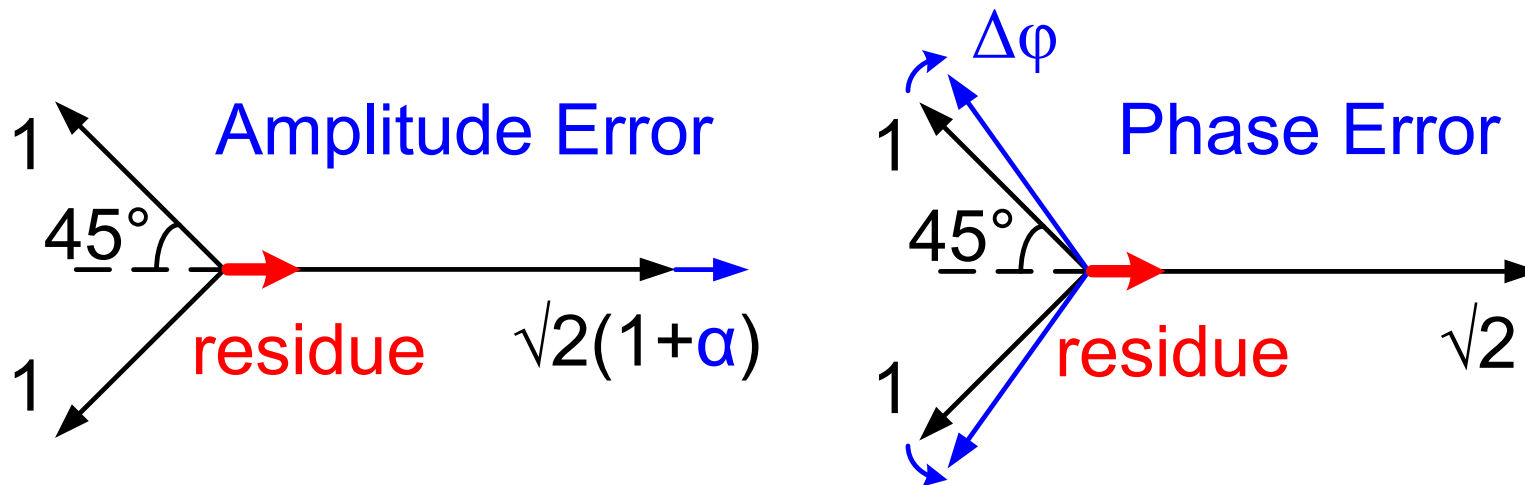


- Amplitude and phase errors
- unwanted harmonic residue → degrade HR ratio
- How to make irrational ratio, e.g. $\sqrt{2}$, on chip?

2-Stage Polyphase HR: Concept

 


• $41/29=1.4138, \sqrt{2}=1.4142 \rightarrow \underline{\underline{\epsilon=0.03\%}}$

2-Stage Polyphase HR: Realization

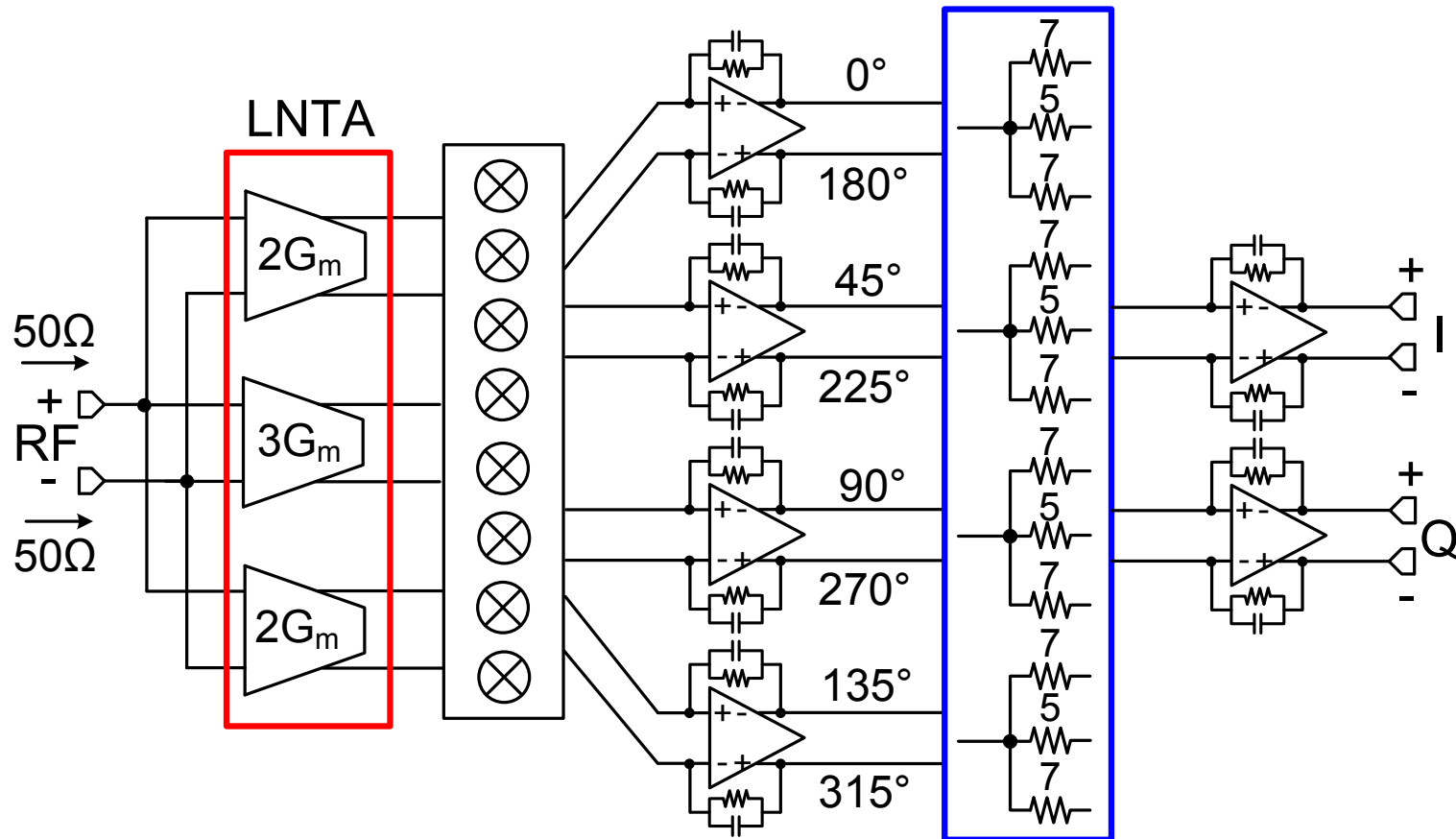


- RF LNTA for 1st-stage weighting (2:3:2)
- BB resistor for 2nd-stage weighting (5:7:5)
- Nominally $\sqrt{2}$, what about influence of mismatch?

Reduced Effect of Amplitude Mismatch

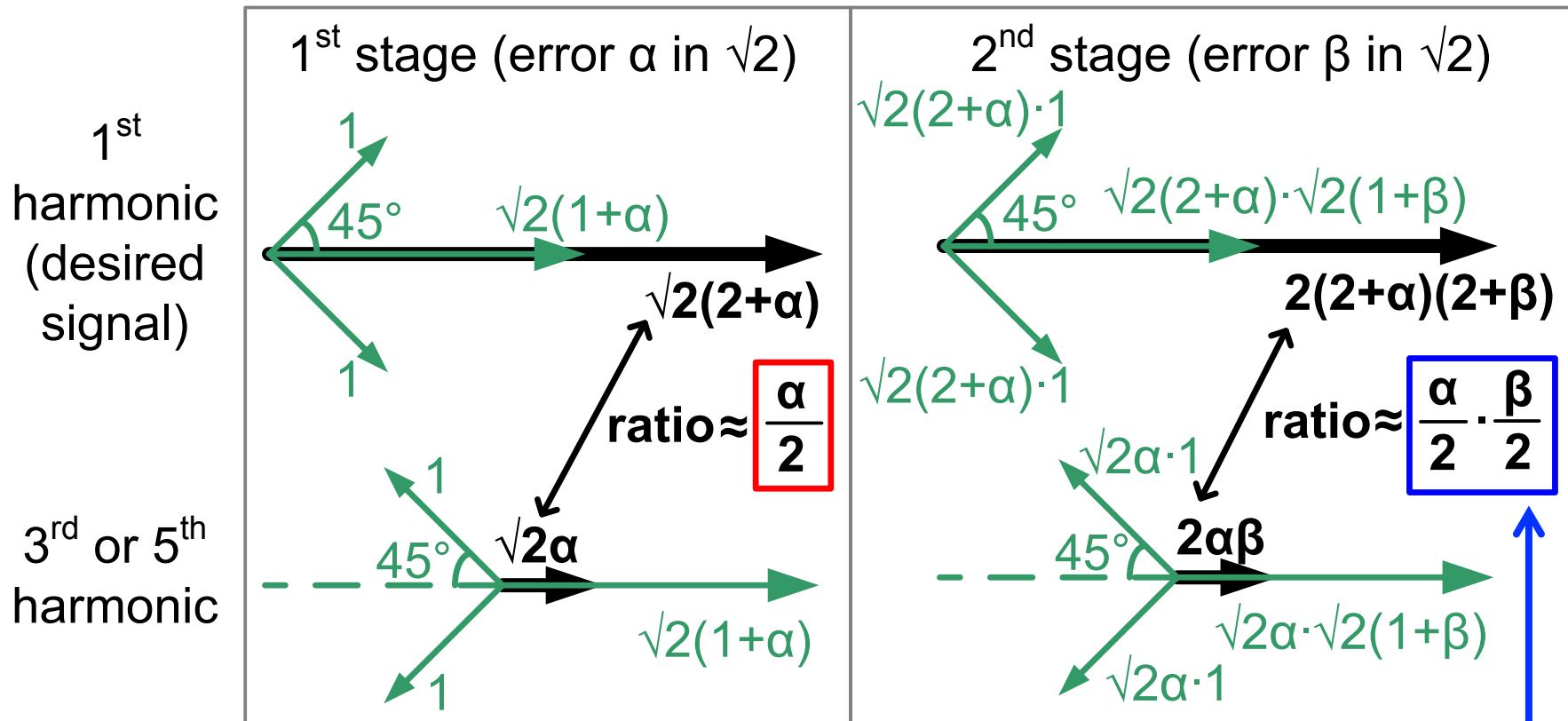


- 2-stage polyphase \rightarrow product of relative errors
- E.g. 2:3:2 $\rightarrow \alpha=6\% \rightarrow$ 1st-stage only: HR3=40dB
 5:7:5 $\rightarrow \beta=1\% \rightarrow$ 2-stage total: HR3=86dB

Zero-IF Receiver Prototype

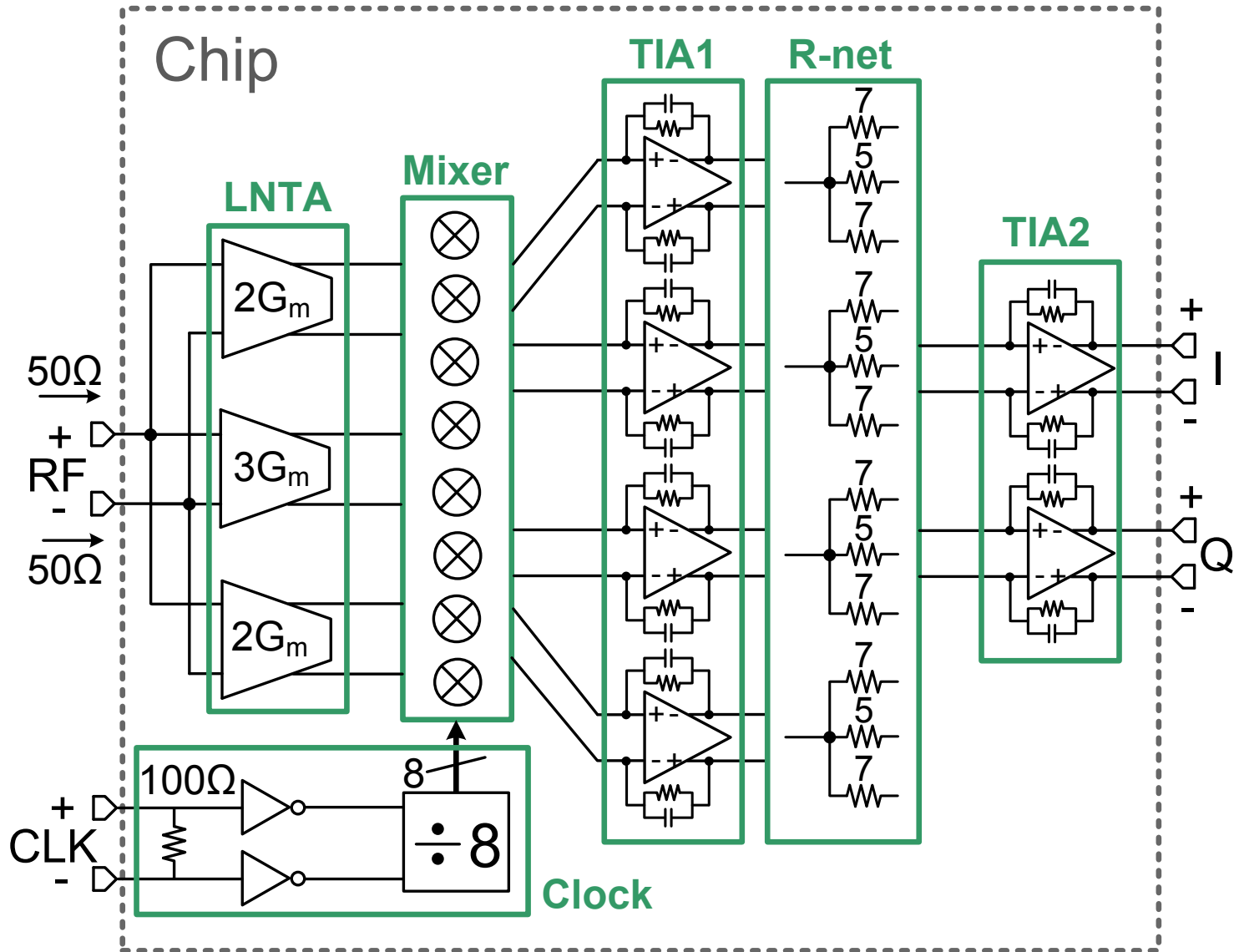


Chip Photo

 

- 1mm² in 65nm CMOS
- VDD: 1.2V
- Current consumption:
 - Analog 33mA
 - Digital 17mA

Measured HR: 40 Chips

HR Ratio @ 0.8G LO

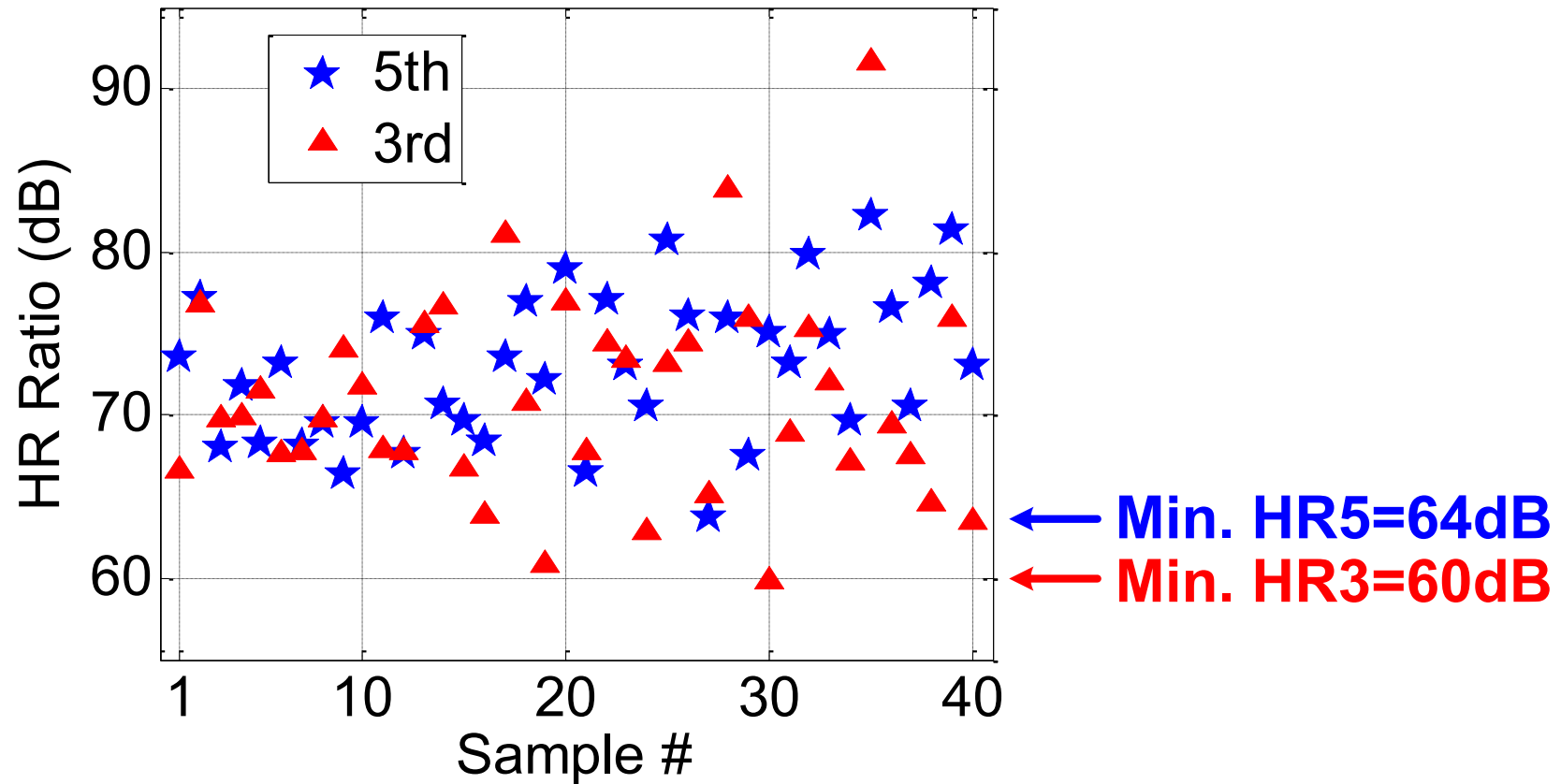

- **No trimming & calibration, no RF filtering**

Measured Performance Summary

LO Frequency	0.4~0.9GHz
Gain	34.4±0.2dB
DSB NF	4dB±0.5dB
$S_{11} < -10$ dB	80M~5.5GHz
In/Out-of-band IIP3 ¹	+3dBm / +18dBm
In/Out-of-band IIP2 ²	+46dBm / +51dBm
IF Bandwidth	12MHz
1/f noise	30kHz corner

VDD	1.2V
Current Consumption	Analog: 33mA
	Digital (clock): 8mA @ 0.4GHz 17mA @ 0.9GHz

Harmonic Rejection Ratio @ 0.8GHz LO	
3 rd -order	> 60dB (40 chips)
5 th -order	> 64dB (40 chips)
2 nd , 4 th , 6 th	> 62dB (20 chips)

¹ Out-of-band IIP3: two tones = 1.61G & 2.40GHz, LO = 819MHz

² Out-of-band IIP2: two tones = 1.80G & 2.40GHz, LO = 601MHz

Outline


- Introduction
- Interferer robust SDR RX – analog part
- **Interferer robust SDR RX – digital part**
- Mixer-first RX
- N-path RF filter
- Interferer scrambler for Software Radio

The Digital approach:

Harmonic Rejection Exploiting Adaptive
Interference Cancellation


[Moseley, ISSCC 2009]

Harmonic Rejection RX: This work

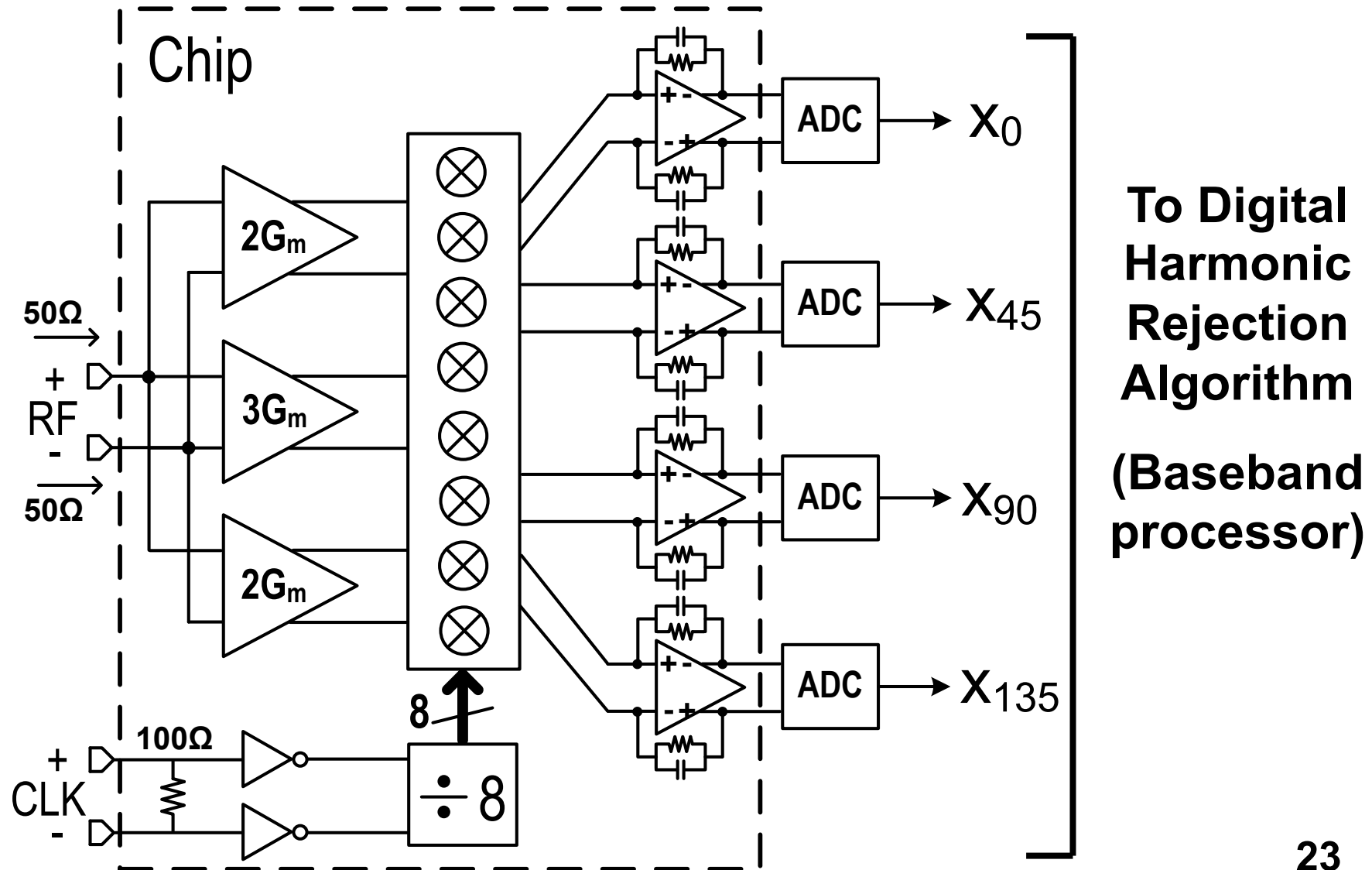


The Basic Idea

 Subtract interference
(residual harmonic image responses)
from received signal.




- **Need *interference estimate signal*.**

Adaptive Interference Cancelling (AIC)



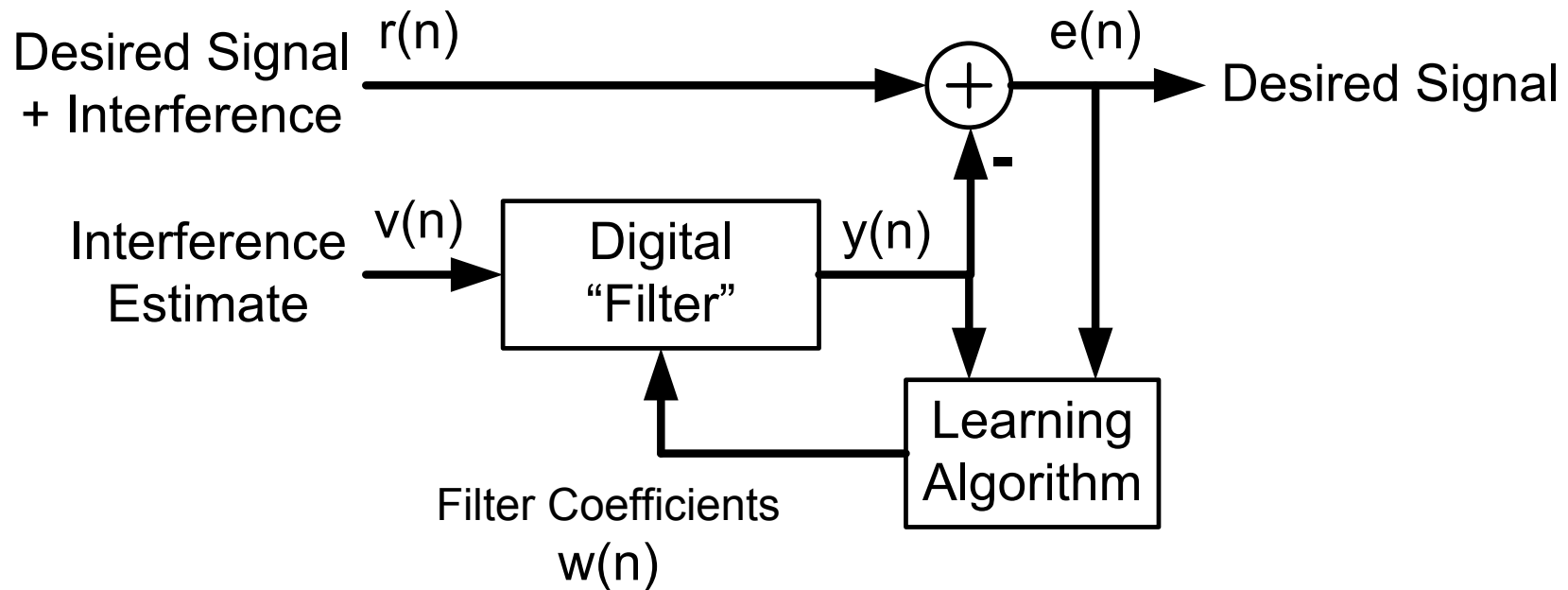


- Adaptive "filter" aligns phase & amplitude.
- Minimizes cross-correlation $v(n)$ and $e(n)$.


Two I/Q signals

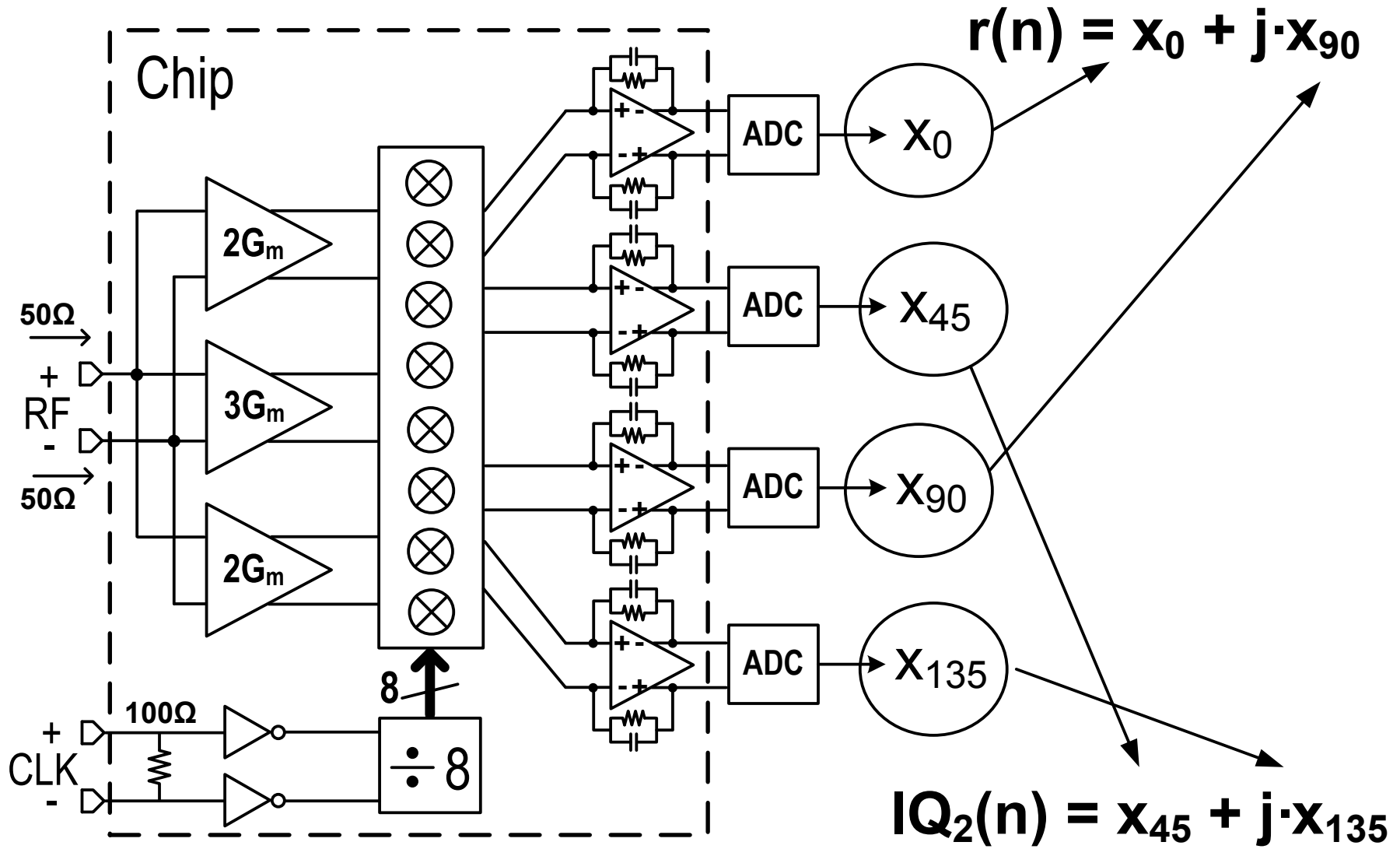


Interference estimate

   


AIC Algorithm 5/5

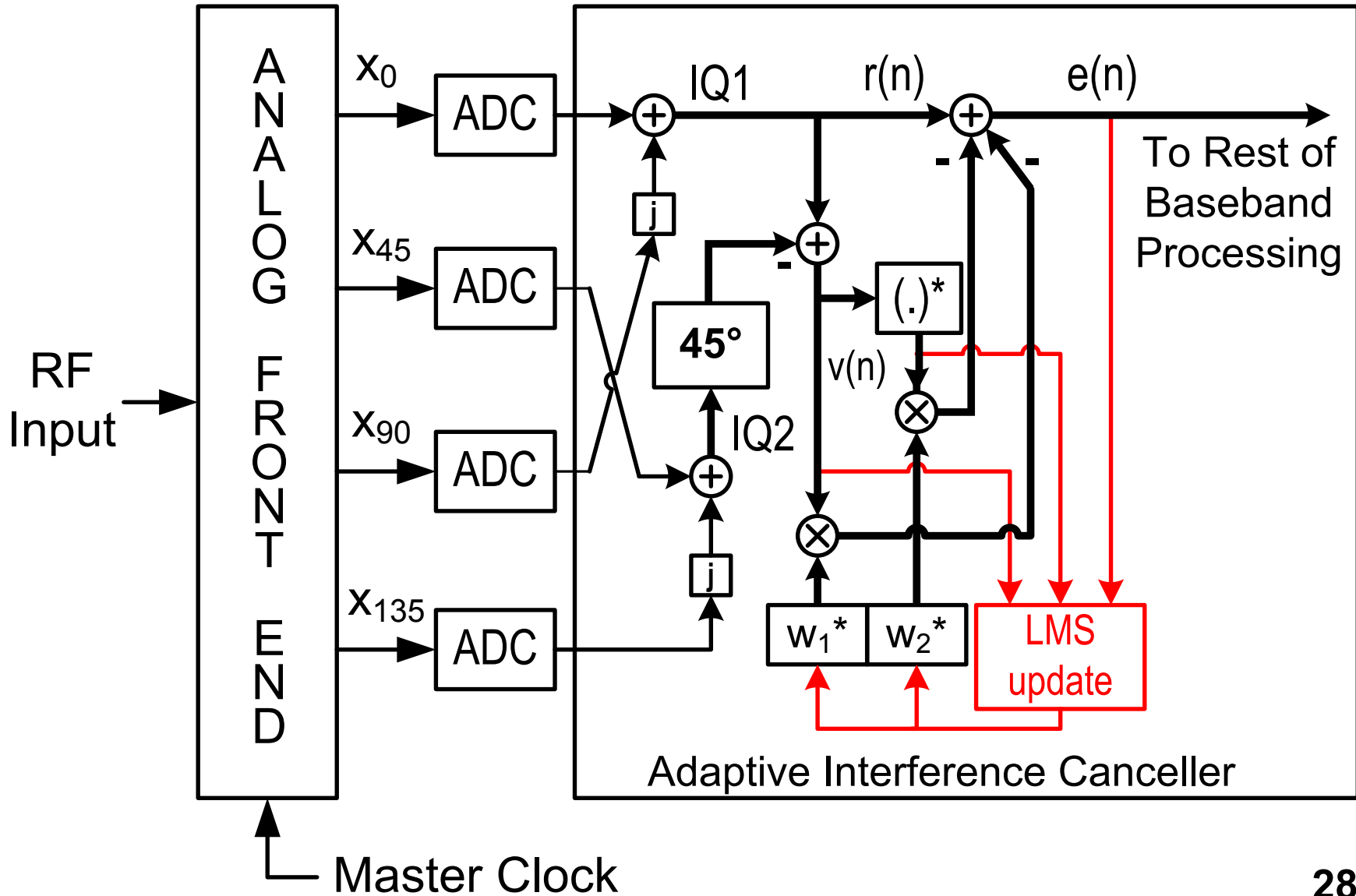


Demonstration

 


Demonstration

 


Demonstration

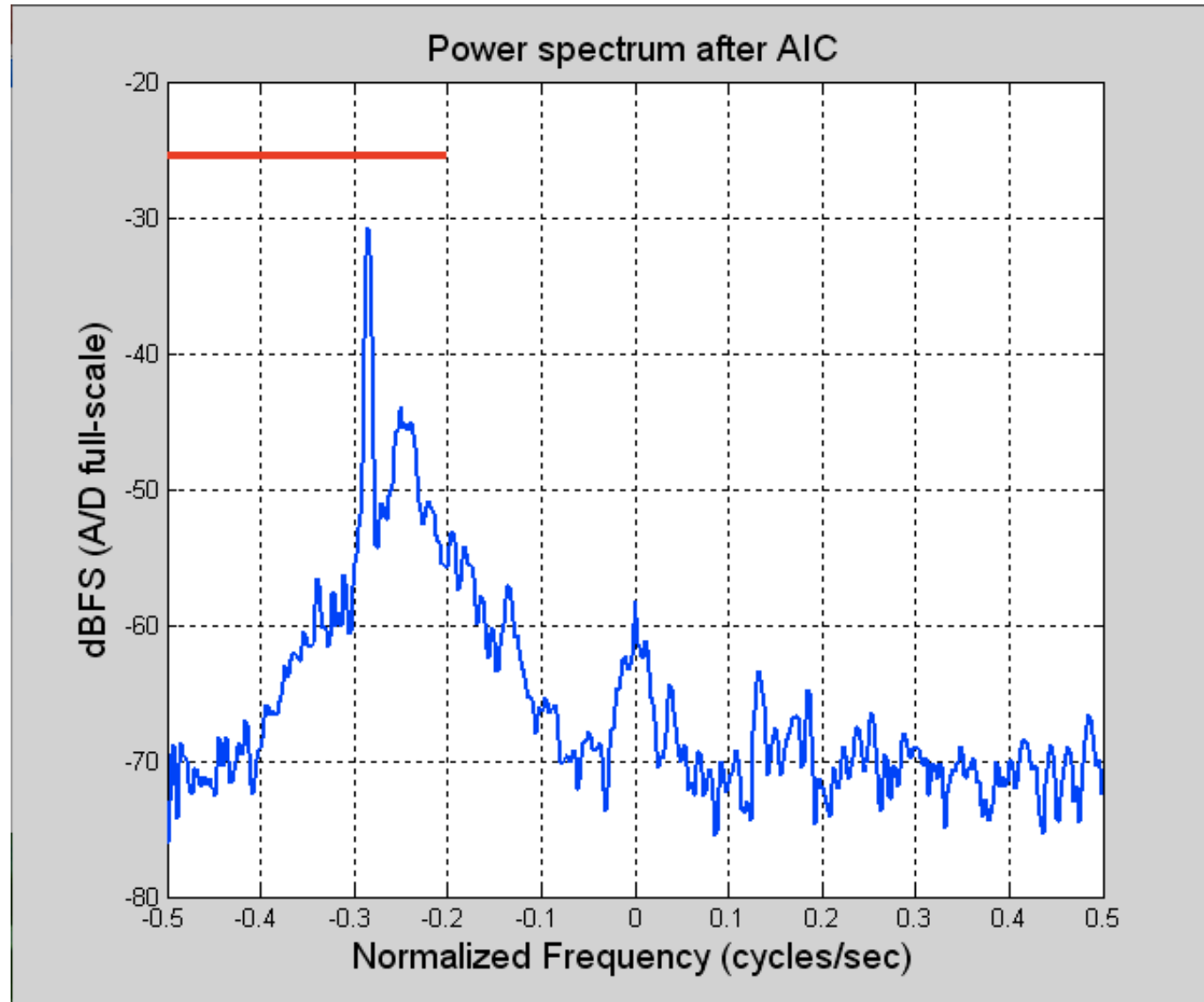

Demonstration

 

Demonstration

 

Comparison

	This work	Z. Ru ISSCC 2009 12.8
Rej. strongest	>80 dB ⁽¹⁾	>60 dB
Rej. other odd	>36 dB	>60 dB
Rej. even	>64 dB	>62 dB
Power frontend	45 mA @ 1.2 V (excl. ADCs)	50 mA @ 1.2 V (excl. ADCs)
Power DSP (100 Msps)	<8.5 mA @ 1.2 V (simulated)	N/A
# ADCs	4 / 2 if AIC off	2

(1) If one harmonic interference image band is dominating.

Outline


- Introduction
- Interferer robust SDR RX – analog part
- Interferer robust SDR RX – digital part
- **Mixer-first RX**
- N-path RF filter
- Interferer scrambler for Software Radio

Mixer-first receiver:

A 0.2-to-2.0GHz 65nm CMOS
Receiver Without LNA Achieving
>11dBm IIP3 and <6.5dB NF

[Soer, ISSCC2009]

Proposed Architecture

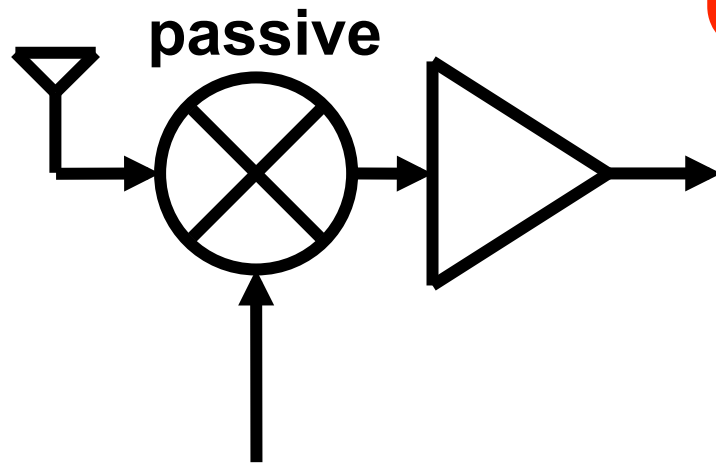

Use passive mixer:

- High linearity



No voltage gain before mixer:

- Noise folding?
- Conversion loss?




Solve with:

- Harmonic cancellation
- Optimized mixer duty cycle





Mixer Operation

 


Linear Periodically Time Variant:

- LO frequency f_s
- Convolution with harmonics (not all shown)
- Noise folding \Rightarrow increases NF

Switching vs. Sampling Mixer

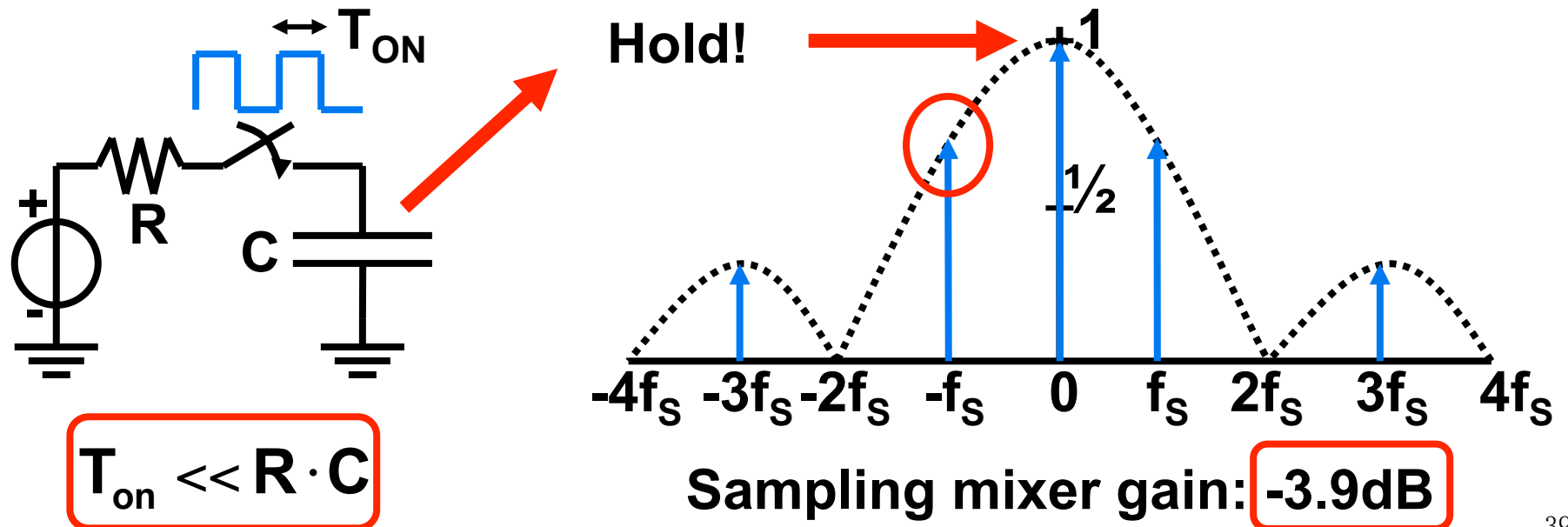 


Multiphase

 

Balanced:



 
- 180° clock phase difference
- No feed-through
- Cancel even-order harmonics



In-phase / Quadrature:

- 90° clock phase difference
- Image rejection?
- Clocks overlap!

25% Quadrature Sampling Mixer

 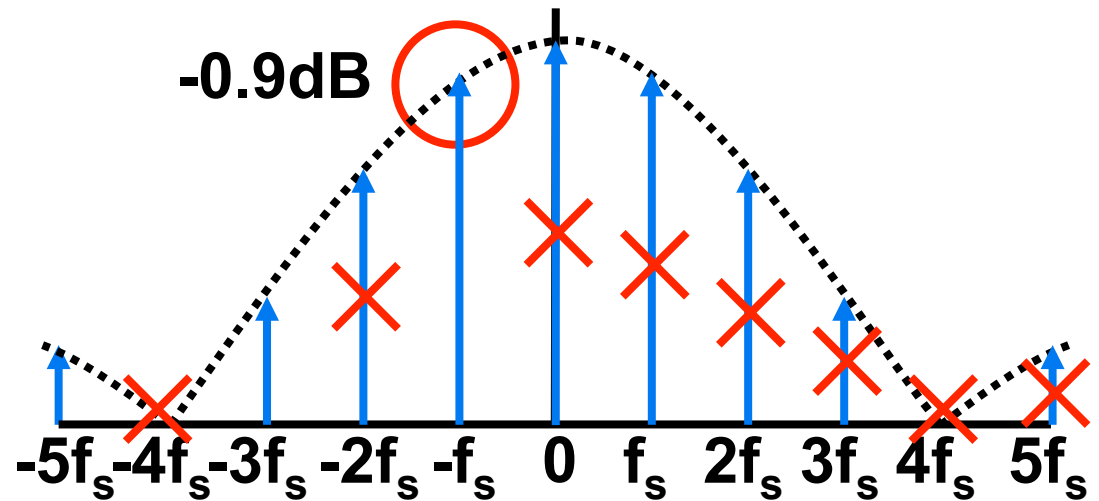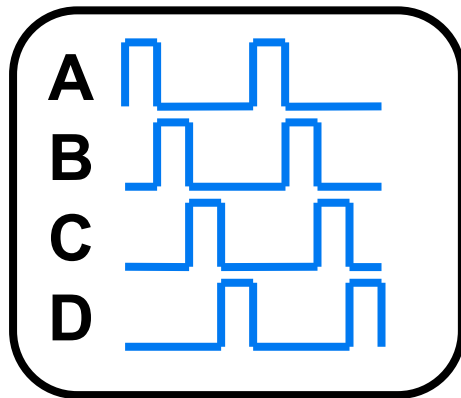

Balanced ✓

I/Q image rejection ✓

-0.9dB conversion gain
0.9dB NF


Total Design

Single-Ended
to
Differential

Differential

Four-phase
Clocks


Differential

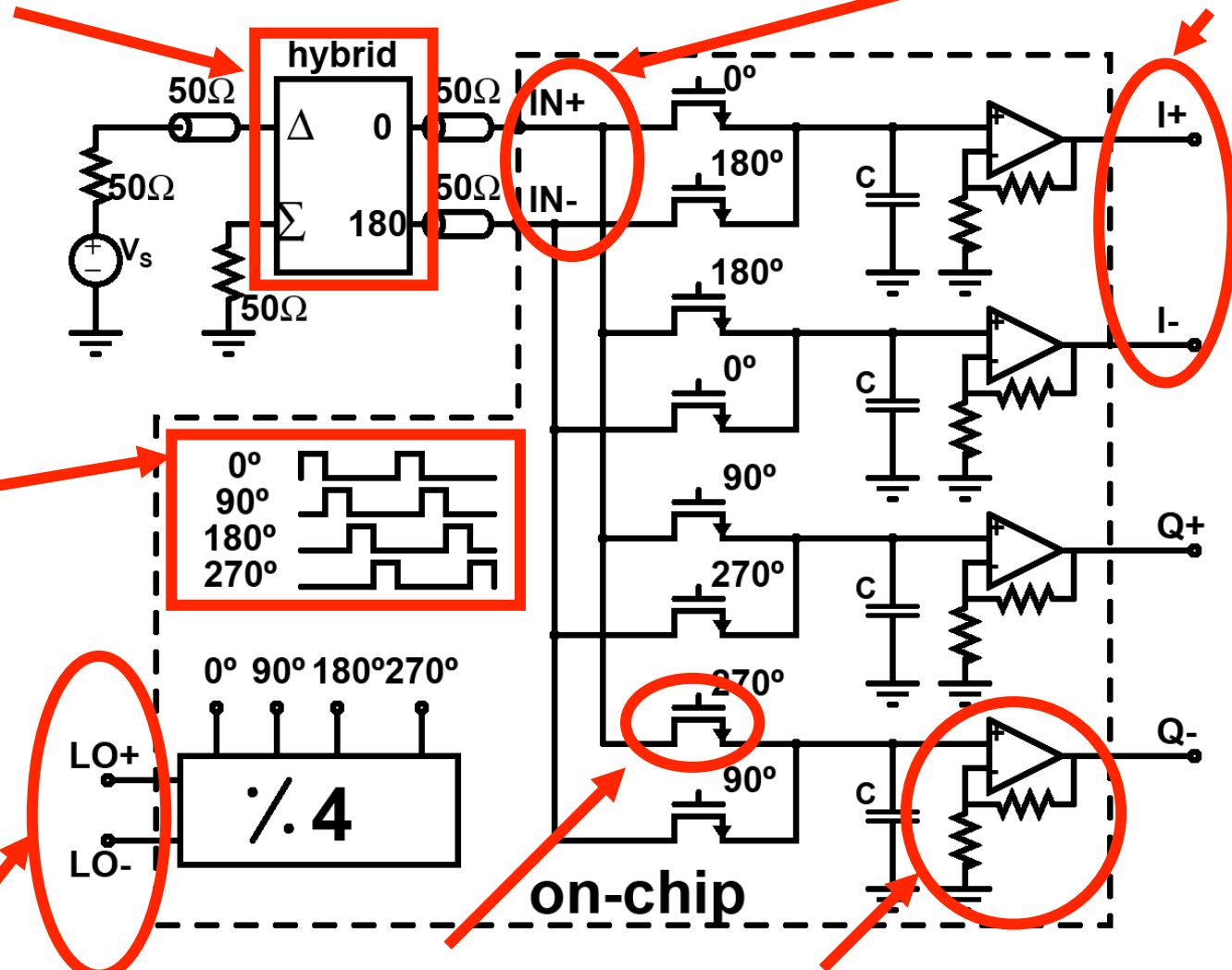

5 Ω Switches

Feedback Amplifier

Chip Micrograph

 

65nm CMOS, active area 0.13mm²

Results & Benchmark


	This Work	[Bagheri, ISSCC 2006]	[van de Beek, ISSCC 2008]	Tektronix RSA2200A	
RF Frequency	0.2 - 2.0	0.8 - 6	0.6 - 10	0 - 3	GHz
IF -3dB Bandwidth	25	20	264	~10	MHz
Gain	19	20	14		dB
DSB NF	6.5	5	7	24	dB
IIP2	+65	+60	+20		dBm
IIP3	+11	-4	0	+30	dBm
SFDR in 1MHz BW	79	70	71	80	dB
Power Dissipation	67	60	90		mW
Supply Voltage	1.2	2.5	1.2		V
Active Area	< 0.13	3.8	< 0.2		mm ²
Technology	65nm	90nm	45nm		CMOS

Outline








- Introduction
- Interferer robust SDR RX – analog part
- Interferer robust SDR RX – digital part
- Mixer-first RX
- **N-path RF filter**
- Interferer scrambler for Software Radio

Idea from 1960: N-Path Filters

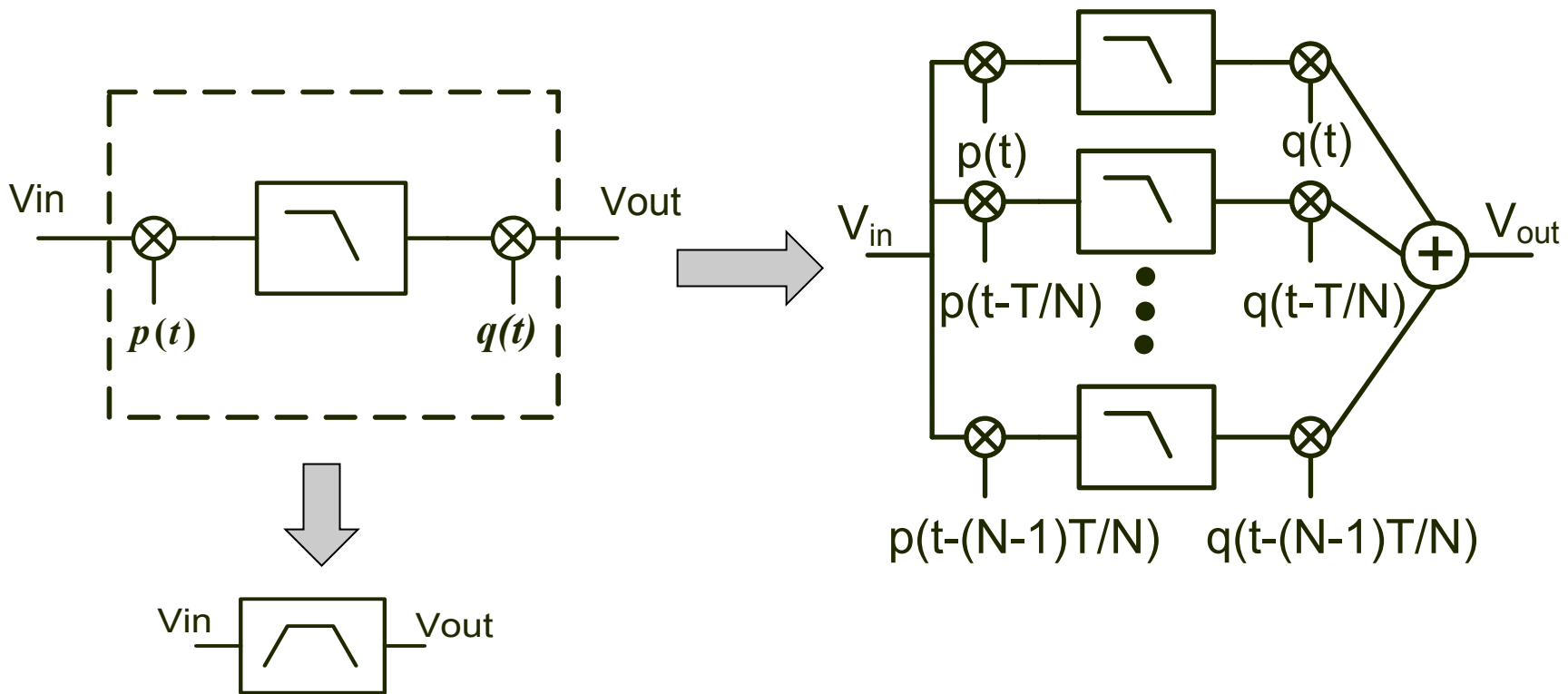- Downconvert & LPF & Upconvert = BPF
- Square-wave clock, harmonic mix problem
 - Cancel using multiple paths!





Simple Implementation

       

Operation:

$RC \gg T_{on}$

 
 


[Franks-ISSCC60]
"N-path filters"

- High ohmic @ switching frequency
- Short circuit @ other frequencies


Filter Properties

 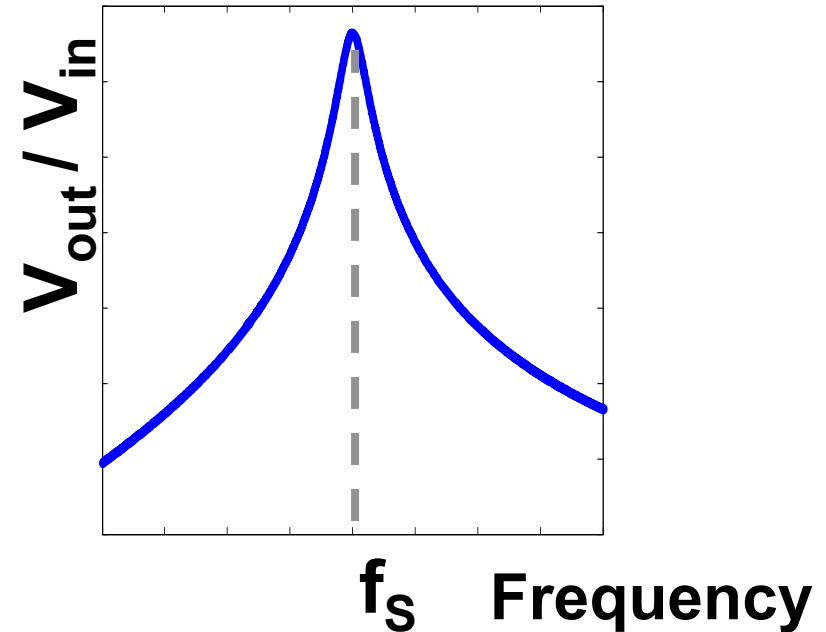- Band-pass around f_s
- Tunable (clock f_s)
- High Q for high $RC \cdot f_s$
- Good linearity & noise
- Unwanted harmonics




More paths \Leftrightarrow Less Distortion

Filter Properties: flexibly tunable

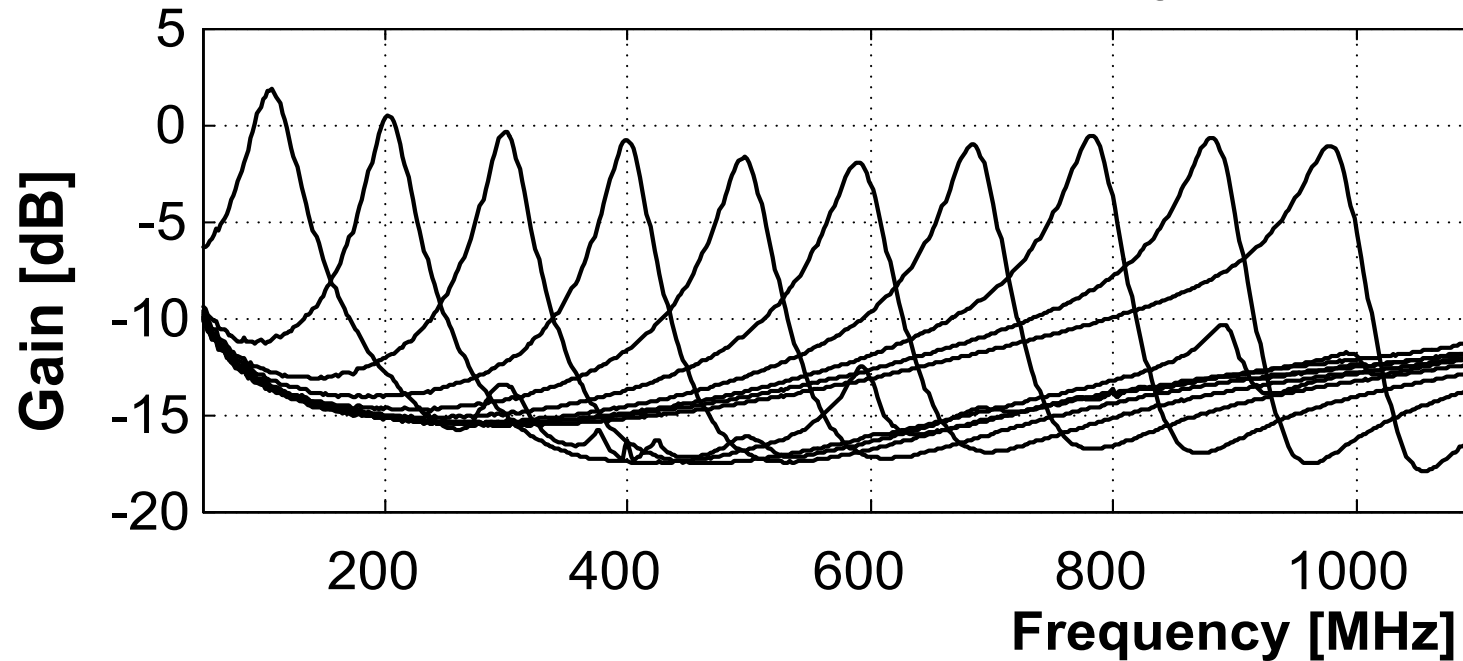

Selectivity (Q)	3 to 29
Compression (P_{1dB})	+2dBm
Linearity (IIP3)	+19dBm
Noise Figure	<5.5dB
Power	2-16 mW

65nm CMOS chip*

 


[Ghaffari, Klumperink, Nauta-RFIC10-JSSC5-2011]

Outline


- Introduction
- Interferer robust SDR RX – analog part
- Interferer robust SDR RX – digital part
- Mixer-first RX
- N-path RF filter
- **Interferer scrambler for Software Radio**

Interferer scrambling for Software Radio

 - Software defined radio
- Problem: linearity ADC





→ in-band harmonic: SNDR ↓

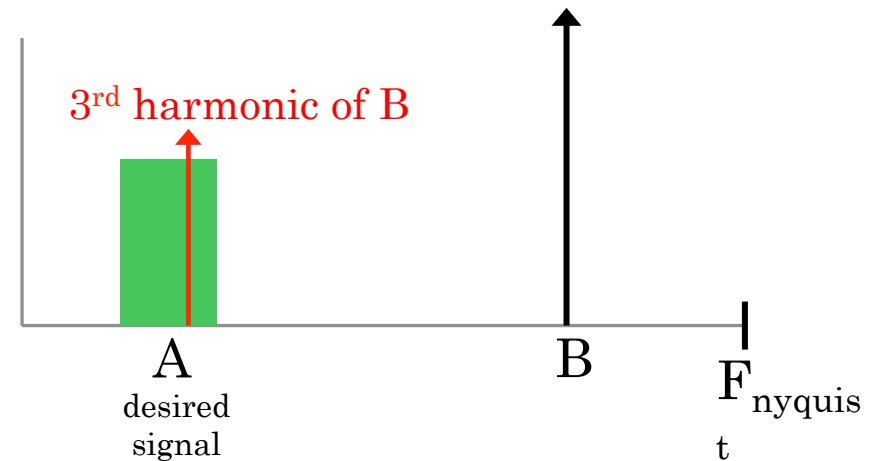



Introduction

- proposed solution: scrambling

  



Scrambling Concept

- proposed solution: scrambling

  



Scrambling Concept

- proposed solution: scrambling

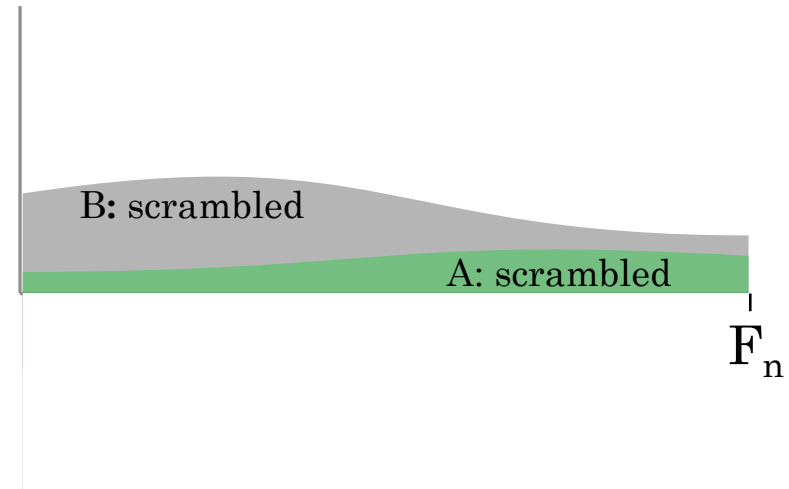 


Scrambling Concept

- proposed solution: scrambling

  


Scrambling Concept

- proposed solution: scrambling

 


→ distortion now wideband

 


Scrambling Concept


- proposed solution: scrambling

 

- After recovery
→ In-band SNDR improved

 





Scrambling Concept

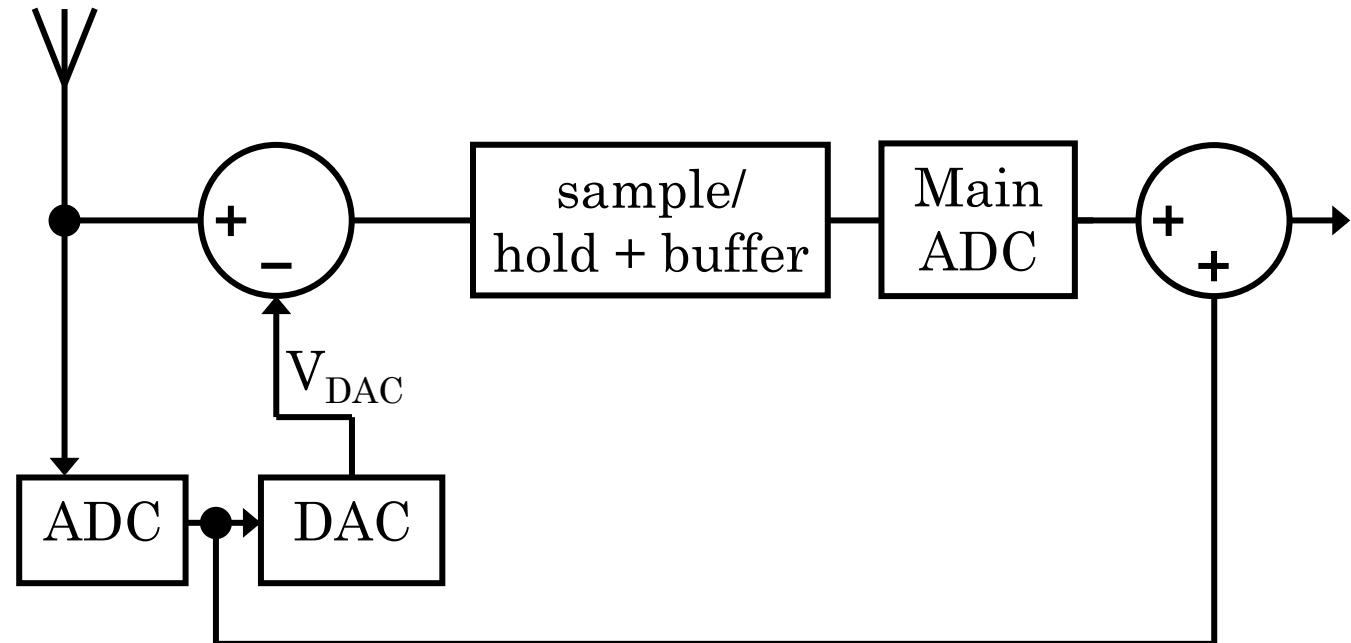

- Challenges:
 - DAC performance
 - Subtractor performance
 - phase alignment
- Solutions presented at ESSCIRC 2011





Matlab example; 1 Gs/s main ADC, 1 MHz input sine

$$y(t) \approx x(t) + 0.01x^3(t)$$

    


Matlab example; 1 Gs/s main ADC, 1 MHz input sine

$$y(t) \approx x(t) + 0.01x^3(t)$$

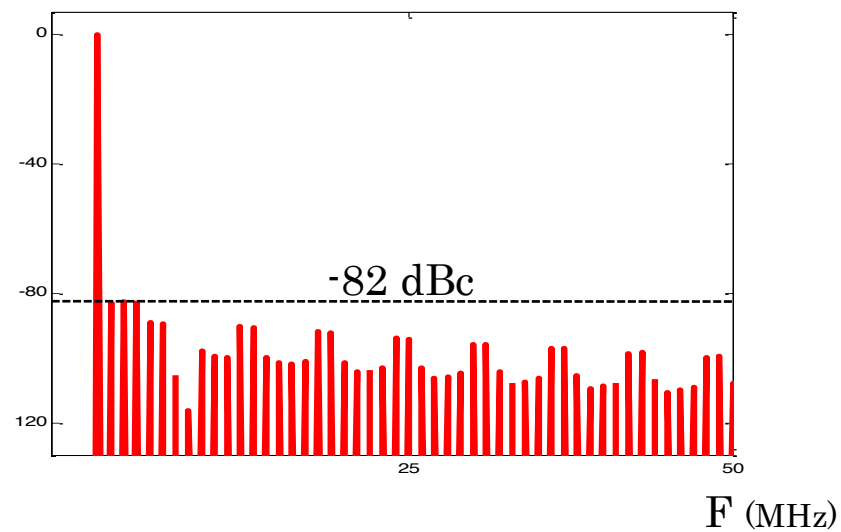   


 Die photo (total 5 mm², bolt-on circuit = 0.27 mm²)



Measurements

$f_s=800$ Ms/s,

 

Summary

- Interferer robust RX
 - No voltage gain @ RF
 - **Filter** before voltage gain
 - HR: error of errors
- Digital Harmonic Rejection RX
 - **Adaptively** kills the biggest harmonic interferer

Summary

- Mixer-first RX
 - Very **linear**
 - Reasonably low noise without LNA
- N-path RF filter
 - very **linear**
 - high Q

Summary

- Interferer scrambler
 - Relaxes ADC design (linearity)
 - 2 bits extra input swing + better SFDR