 




2014 SoS Workshop Mixed-Signal IC Design

Presented by Pietro Andreani

Department for Electrical and Information Technology
Lund University




Work performed in 2013-2014

- Filtering CT $\Delta\Sigma$ ACSs for LTE
 - Mattias Andersson
- An ultra-low-power CT $\Delta\Sigma$ ADC with SAR quantizer
 - Dejan Radjen (simulations)
- CT $\Delta\Sigma$ ADC for LTE
 - Xiaodong Liu (not shown)
- A digital PLL
 - Ping Lu (simulations)
- Two class-D VCOs
 - Luca Fanori
- A reconfigurable wideband VCO
 - Ahmed Mahmoud (not shown)


Merging LPF and ADC

Mattias Andersson

 


Channel-Select Filter + CT $\Delta\Sigma$ ADC

Tow-Thomas
2nd-order CSF

 

Noise from DSM is 2nd-order shaped by global feedback


ESSCIRC '13
SoS workshop '13

 


Improved Version: Filtering CT $\Delta\Sigma$ ADC Supporting LTE 2x20MHz

3rd-order CSF

2nd-order DSM

 


JCCS July 2014

 


Noise from DSM shaped by three zeroes in CSF

Simulation with white noise at DSM input

 


DSM noise suppressed by three zeroes \rightarrow 19dB gained!

Filtering ADC

 

- 3rd-order Chebychev CSF, 9.0/18.5 MHz BW
- 2nd-order DSM, 3-bit DACs, $f_s=288/576$ MHz

 
Filtering ADC vs plain $\Delta\Sigma$ ADC



Topologically identical! – However:


- 5th-order DSM
 - 5 poles at high frequencies to maximize SQNR
- Filtering ADC:
 - 2 poles at low frequencies for filtering
 - 3 poles at high frequencies for SQNR

Chip photograph

 


- ST 65nm CMOS
- $V_{dd}=1.2V$, $I_{dd}=9.4mA$ (11.3mW)
- $f_s=288MHz$, $BW=9MHz$
- Core area $0.5 \times 0.22mm^2$

Signal Transfer Function in 2xLTE20

 


SNR and SNDR in 2xLTE20

 


Tolerance to blockers, 2xLTE20

5MHz SC-FDMA blockers

 


CW blockers

 


- P_{1dB} vs. blockers (P_{1dB} = blocker power for which in-band noise increases by 1dB)
- Assuming 10mS front-end and -54dB TX-to-RX in duplexer

Tolerance to blockers, LTE20

5MHz SC-FDMA blockers

 

CW blockers

 


- P_{1dB} vs. blockers
- Assuming 10mS front-end and -54dB TX-to-RX in duplexer

State-of-the-art in filtering ADCs

Parameter	Paper V	Paper IV	Philips ISSCC'04	Sosio ESSCIRC'11	Rajan ISSCC'14
fs (MHz)	576	288	64	405	256
BW (MHz)	18.5	9	1	6	2
SNDR (dB)	56.4	68.4	59	74.6	74.4
Filter order	3	2	1	2	2
Avg. IRN in BW (nV/ $\sqrt{\text{Hz}}$)	5.1	8.1	280	–	40
Gain setting (dB)	26	12	0	–	0
In-band IIP3 (dBV _{rms})	-8.5	11.5	19	–	24
Out-of-band IIP3 (dBV _{rms})	20	27	–	–	34
f _{-3dB} (MHz)	25.0	16.9	3	–	4
Power (mW)	7.9	11.3	2	54	5
Tech. (nm)	65	65	180	90	130
Vdd (V)	1.2	1.2	1.8	1.2-1.8	1.4
DR at BW×4 (dB)	82	80	65	90	90.5
FOM1 at BW×4 (fJ/c.)	21	77	700	180	45
FOM2, OOB IIP3 (aJ)	4	7	–	–	15


A 2nd-order CT $\Delta\Sigma$ modulator with an SAR quantizer

Dejan Radjen

 


Part of a large SSF project, "Wireless Communication for Ultra Portable Devices (UPD)", lead by Prof. Henrik Sjöland

Architecture of $\Delta\Sigma$ modulator

 


- $\Delta\Sigma$ modulator with a 4-bit SAR quantizer
- SAR more power efficient than standard flash quantizers
- Generation of clock at $5f_s$ avoided with asynchronous control

Details of $\Delta\Sigma$ modulator

 

- 2nd-order loop filter with single opamp to save power
- Resistive feedback DACs with NRZ pulses

Simulation results

 


Performance summary	
Parameter	Simulated performance
Technology	65 nm CMOS
Supply voltage	800 mV
Signal bandwidth	500 kHz
Maximum input amplitude	200 mV differential
Clock frequency	16 MHz
SNDR	65 dB
Power consumption	69 μ W
Figure of merit	47 fJ/conv


- Unfortunately, unstable in real life due to impact of layout parasitics
- Redesign ongoing

Digital PLL

Ping Lu

 


Digital PLL

 


Time-to-digital converter (TDC)

2-D gated-ring-oscillator (GRO) Vernier TDC


RFIC 2013

 

 
- GRO \rightarrow shaping of quantization noise
- 2-D \rightarrow large detection range, low latency



Class-D DCO

 


Noise cancellation

 


Cancellation off

Cancellation on

 


Phase noise simulations

 


- BW=1.1MHz
- Noise cancellation strongly reduces quantization noise
- Waiting for IC to return from fab

VCOs

 

Luca Fanori &
Thomas Mattsson
(Ericsson)

Prior art: class-D oscillator

 


ISSCC 2013, JSSC Dec. 2013

- Amplitude $A \approx 3V_{dd}$, efficiency $> 90\%$
- Excellent switches available in nm CMOS
- Suitable for very low V_{dd}


1st VCO: dual-core VCO with $TR > 1$ octave

ISSCC 2014

 


- Orthogonal 8-shaped inductor \rightarrow no magnetic field between coils
- Very wide tuning range with small inductor area
- Class-D \rightarrow low voltage supply, high performance

Chip photograph

 


- 65nm CMOS process without thick metal
- Inductors: 1nH and 0.6nH
- Overall tuning range: 2.4-5.3GHz (75%)
- 0.33mm² active area
- Voltage supply: 0.4-0.5V

Tuning range

 


Q vs. frequency

 


- (1) Actual design
- (2) Other inductor removed (difference < 10%)
- (3) Inductor optimized for standalone VCO

Phase noise at $V_{dd} = 0.5V$

 


- FoM $\approx 188/189$ dBc/Hz across the tuning range
- 1/f³ noise corner frequency between 0.7 MHz and 1.5 MHz

Chip photograph

 

- 65nm CMOS with thick top metal
- 0.9nH inductor
- $Q_{\text{ind}} = 14$, $Q_{\text{tank}} = 11$ @ 4GHz
- Tuning range: 3.0 – 4.3GHz
- Area: $850\mu\text{m} \times 410\mu\text{m}$
- $V_{\text{dd}} = 0.4\text{-}0.5\text{V}$
- $V_{\text{dd,ext}} = V_{\text{dd}} + 200\text{mV}$

Phase noise at $V_{dd} = 0.5V$

 



LUND
UNIVERSITY

**SCANDINAVIAN EXCELLENCE
DEFINED IN LUND**

